

Implementation of Combinational Logic Circuits

$$F = \underbrace{L_1 + \dots + L_m}_{m \text{ literals}} + \underbrace{P_1 + \dots + P_k}_{k \text{ products}} \quad \text{SOP}$$

NAND is complete, hence SOP can be implemented with NAND alone



$$(F')' = (L_1' L_2' \dots L_m' P_1' \dots P_k')' = F$$

Example:

$x_3 x_4$ $x_1 x_2$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	1
10	0	1	1	0

$$F = x_1 x_2 x_3 + x_4$$
  
$$F = (x_3 + x_4)(x_1 + x_4) \cdot (x_2 + x_4)$$





$$F = \underbrace{L_1 L_2 \dots L_m}_{m \text{ literals}} \underbrace{S_1 S_2 \dots S_k}_{k \text{ sums}}$$

POS

NOR is complete
  
$$F = (F')' = (L_1' + L_2' + \dots + L_m' + S_1' + S_2' + \dots + S_k')$$



Multilevel Circuit Implementation

Propagation delay. 2-level is the fastest.



Fan-in limit

Example: $F = x_1 x_2 + x_1 x_3' + x_2 x_3 x_4$

Fan-in is 3, We'd like Fan-in 2 implementation

 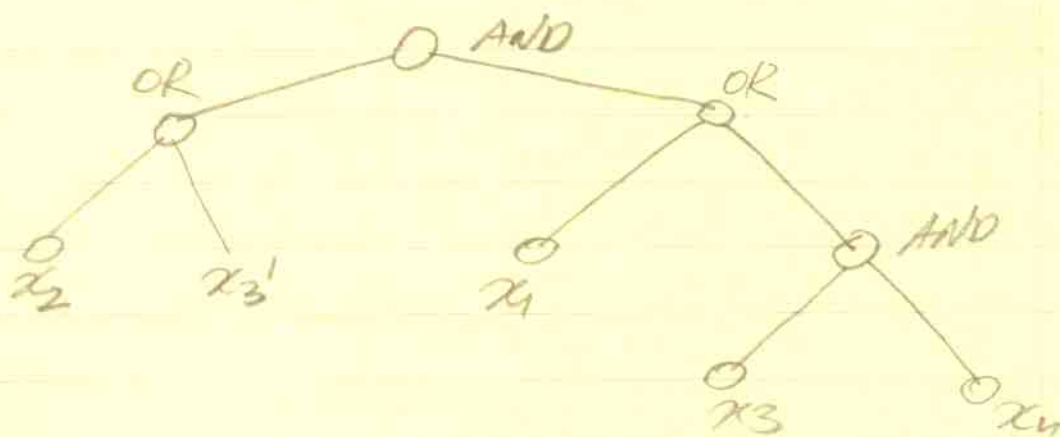Problematic - 60-
Problematic

$$F = x_1x_2 + x_1x_3' + x_2x_3x_4 = x_1(x_2 + x_3') + x_2x_3x_4 + x_3x_3'x_4 = x_1(x_2 + x_3') + x_3x_4(x_2 + x_3') = (x_2 + x_3')(x_1 + x_3x_4) \quad \text{O.K.!}$$



Multilevel NAND (NOR) Circuits

- ① Obtain minimal SOP (POS)
- ② Factor SOP to satisfy fan-in limit
(POS) (AND)
- ③ Make output OR traverse backwards
AND-OR alternating
(OR-AND)

④ Replace all gates with NAND (NOR)

⑤ Complement all inputs originally input to OR (AND)

Example: Implement with NOR and fan-in ≤ 3
 $F = \Sigma(0, 3, 4, 5, 8, 9, 10, 14, 15)$

$x_1 x_2$ \ $x_3 x_4$	00	01	11	10
00	1	0	1	0
01	1	1	0	0
11	0	0	1	1
10	1	1	0	1


$$F = (x_1' + x_2' + x_3) \underbrace{(x_1 + x_2 + x_3 + x_4')}_{\text{factor } x_2 + x_4'} \underbrace{(x_1' + x_2 + x_3' + x_4')}_{\text{factor } x_1 + x_3'} (x_1 + x_2' + x_3')$$

AND: 5 fan-in, 2 OR: 4-fan-in

$$= (x_1' + x_2' + x_3) \left[(x_2 + x_4') + (x_1 + x_3)(x_1' + x_3') \right]$$


$$\left[(x_1 + x_3') + x_2' x_4 \right]$$

 We obtained products and sums of 3 at most



Arithmetic Circuits


Full adder

 

$$S = x \oplus y \oplus z$$

$$G = (x \oplus y)z + xy = [(x \oplus y)z]'(xy)']'$$

NAND implementation

 

Example : Binary to gray code converter

In gray code successive decimal numbers are coded such that they differ on 1-bit only

Decimal	Binary	Gray
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
	⋮	
13	1101	1011
14	1110	1001
15	1111	1000

Gray ^{conversion} code of two successive binary is based on the number of successive 01 or 10 in the binary code

The addition of $00 \dots 01$ to a binary number will change by 1 exactly the 01 or 10.

Hence parity check by $\oplus$ will do the work


$b_{n-1} b_{n-2} \dots b_1 b_0$ - binary

$g_{n-1} g_{n-2} \dots g_1 g_0$ - Gray


$$g_i = b_i \oplus b_{i+1} \quad 0 \leq i \leq n-2$$

$$g_{n-1} = b_{n-1}$$

Decimal
45

 


46

 

We can use full adder to implement

The converter

 Homework: prove that obtained gray code is unique



Homework: Design **subtractor** (full)

x - minuend, y - subtrahend, z - borrow

$$x - y - z = x - (y + z)$$

① Write truth table


Inputs			outputs	
x	y	z	borrow	difference
1	1	1	1	1
0	1	1	1	0
0	1	0	1	1
...	...	...	...	...

② K-map

③ Implement

Binary Parallel Adder

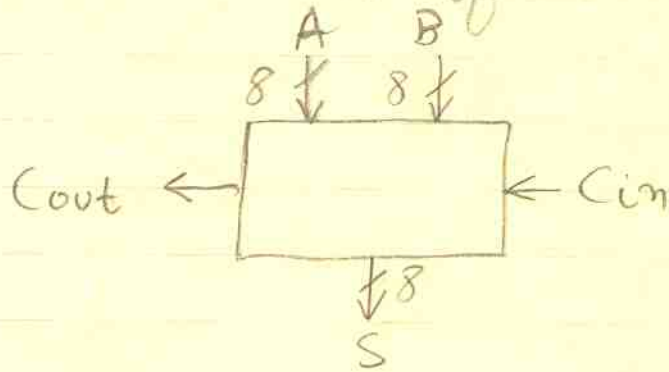
Consider addition of two 8-bit binary numbers



$$A = (a_7 a_6 \dots a_0)$$


$$B = (b_7 b_6 \dots b_0)$$

What is the size of Truth table?

 

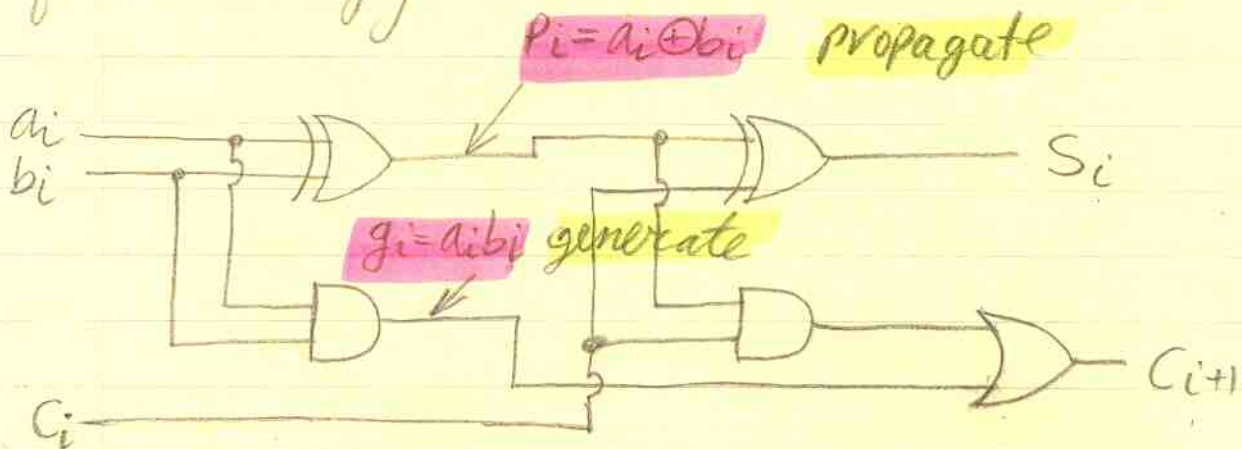Problem: carry propagation

n -bit parallel adder delay is $O(n)$ regardless of technology



The output carry is a sum (OR) of two variables

- 1) $G_i = a_i b_i$ - a carry out is generated if $a_i = 1$ and $b_i = 1$
 - 2) $P_i C_i$, namely the carry in is propagated if $P_i = 1$
- carry independent

$$P_i = a_i \oplus b_i, \quad G_i = a_i b_i$$

$$S_i = P_i \oplus C_i, \quad C_{i+1} = G_i + P_i C_i$$

recursive expression
↙

We could evaluate the carry out of each adder as follows

$$\begin{aligned} C_{i+1} &= G_i + P_i C_i = G_i + P_i (G_{i-1} + P_{i-1} C_{i-1}) = \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} (G_{i-2} + P_{i-2} C_{i-2}) = \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + P_i P_{i-1} P_{i-2} (G_{i-3} + P_{i-3} C_{i-3}) = \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 C_0 \end{aligned}$$

We obtained SOP of known variables


Hardware implementation 3-bit adder

$$C_1 = g_0 + P_0 C_0$$

$$C_2 = g_1 + P_1 g_0 + P_1 P_0 C_0$$


$$C_3 = g_2 + P_2 g_1 + P_2 P_1 g_0 + P_2 P_1 P_0 C_0$$
 
$$C_{i+1} = g_i + \sum_{k=1}^i \left[g_{i-k} \prod_{l=0}^{i-1} P_{i-l} \right] + C_0 \prod_{l=0}^i P_l$$



- 69

Combining everything together

 

and AND trees

Comments:


1- CLA by SOP is $O(1)$ but fan-in limit may require ER trees, hence evaluation time is $O(\log n)$

short Homework

2- Hardware of CLA is big, in fact $O(n \log n)$


Using Adder for Subtraction

 Parallel adder can be used for subtraction by taking the 2's complement of the subtrahend. It is implemented by inverting the bits and adding 1 via the carry in the bits and adding 1 via the carry in



The same unit can perform both addition and subtraction by entering $\bar{b}$ via XOR controlled to pass it unchanged in case of addition or invert it in subtraction

70.1

 

if ($SUBTRACT == 0$)

$$\bar{S} = \bar{a} + \bar{b} \quad (\text{vectors})$$

else

$$\bar{S} = \bar{a} - \bar{b}$$

Carry-Save Addition

Carry look ahead adder adds 2 n -bit numbers in $O(\log_2 n)$ time. Adding 3 n -bit numbers doesn't need two CLA additions!

$$\text{Let } \bar{x} = (x_{n-1}, x_{n-2}, \dots, x_0)$$

$$\bar{y} = (y_{n-1}, y_{n-2}, \dots, y_0)$$

$$\bar{z} = (z_{n-1}, z_{n-2}, \dots, z_0)$$

$$\begin{array}{rcccccccc}
 & \bar{x} & & x_{n-1} & x_{n-2} & \dots & x_i & \dots & x_1 & x_0 \\
 + & \bar{y} & = & + & y_{n-1} & y_{n-2} & \dots & y_i & \dots & y_1 & y_0 \\
 + & \bar{z} & & + & z_{n-1} & z_{n-2} & \dots & z_i & \dots & z_1 & z_0
 \end{array}$$

Consider the addition on bit i . There are two implications:

- The result on s_i is the Parity of x_i, y_i, z_i and the carry from $i-1$
 - The carry c_i is the majority of the above
- Hence, we can represent $x+y+z$ as:

-70.3-

$$x + y + z = u + v, \text{ where}$$


$$u_i = \text{parity}(x_i, y_i, z_i)$$

$$v_{i+1} = \text{majority}(x_i, y_i, z_i)$$

$$v_0 = 0$$

Example:

i	8	7	6	5	4	3	2	1	0
$\bar{x}$		0	0	0	1	1	1	0	1
$\bar{y}$		1	1	0	0	0	1	0	1
$\bar{z}$		1	0	0	1	0	1	1	0
$\bar{u}$		0	1	0	0	1	1	1	0
$\bar{v}$		1	0	0	1	0	1	0	0

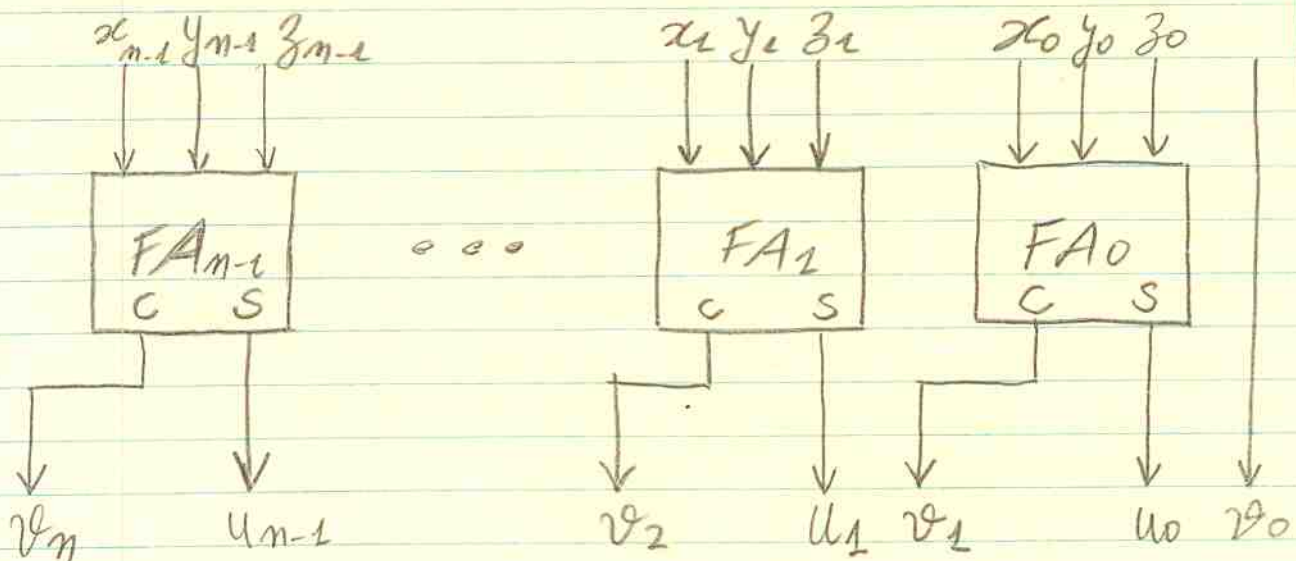

$\bar{u}$ and $\bar{v}$ are then summed by CLA.
Notice that the generation of $\bar{u}$ and $\bar{v}$
takes $O(1)$ time.

Carry-Save adder is useful for fast
multiplication by Wallace-Tree multiplier.

③

71

Multiplier (unsigned)

$$\begin{array}{r}
 x_4 \ x_3 \ x_2 \ x_1 \\
 y_4 \ y_3 \ y_2 \ y_1 \\
 \hline
 x_4 y_1 \ x_3 y_1 \ x_2 y_1 \ x_1 y_1 \\
 x_4 y_2 \ x_3 y_2 \ x_2 y_2 \ x_1 y_2 \\
 x_4 y_3 \ x_3 y_3 \ x_2 y_3 \ x_1 y_3 \\
 x_4 y_4 \ x_3 y_4 \ x_2 y_4 \ x_1 y_4 \\
 \hline
 \end{array}$$


- ① There are 16 partial products $x_i y_j$ $1 \leq i, j \leq 4$
 We'll therefore need 16 AND gates to produce


$$P_{ij} = x_j y_i \quad 1 \leq i, j \leq 4$$

- ② Notice that for k 's column sum there exist

$$k = i + j - 1; k = 1, \dots, 7$$

 We use carry propagate (parallel) addition as follows:



 

-73.1-

2's complement Multiplier

Recall that the most significant bit has negative weight (sign bit), hence some of the ^{partial} products may be negative and must be subtracted.

Let

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i \quad n\text{-bit}$$

$$Y = -y_{m-1}2^{m-1} + \sum_{j=0}^{m-2} y_j 2^j \quad m\text{-bit}$$

$$P = XY = \sum_{i=0}^{n-2} \sum_{j=0}^{m-2} x_i y_j 2^{i+j} +$$

$$+ x_{n-1} y_{m-1} 2^{m+n-2} -$$

$$\left(\sum_{i=0}^{n-2} x_i y_{m-1} 2^{i+m-1} + \sum_{j=0}^{m-2} x_{n-1} y_j 2^{j+n-1} \right)$$

Example: x and y are 4-bit each
result will occupy 7 bits

-73.2-

$$\begin{array}{cccc}
 y_3 & y_2 & y_1 & y_0 \\
 \hline
 x_3 & x_2 & x_1 & x_0
 \end{array}$$

positive $\left\{ \begin{array}{l} \textcircled{1} \quad \begin{array}{ccc} x_0 y_2 & x_0 y_1 & x_0 y_0 \\ x_1 y_2 & x_1 y_1 & x_1 y_0 \\ x_2 y_2 & x_2 y_1 & x_2 y_0 \end{array} \end{array} \right.$

positive $x_3 y_3$

$$\sum_i \left\{ \begin{array}{ccc} \cancel{01} & \cancel{01} & \overline{x_2 y_3} \quad \overline{x_1 y_3} \quad \overline{x_0 y_3} \end{array} \right\}$$

negative

$$\sum_j \left\{ \begin{array}{ccc} \cancel{01} & \cancel{01} & \overline{x_3 y_2} \quad \overline{x_3 y_1} \quad \overline{x_3 y_0} \end{array} \right\}$$

$\textcircled{1}$ $\textcircled{1} \leftarrow$

$\uparrow$
drop

$P_7 \quad P_6 \quad P_5 \quad P_4 \quad P_3 \quad P_2 \quad P_1 \quad P_0$

The reason for adding implicit $n+m+1$ 'th bit (in this case 7-th bit) is because the result of multiplication of $(n+1)$ -bit and $(m+1)$ -bit numbers is obtained in $n+m+1$ bits.

-73.3-

$$\begin{array}{cccc} & y_3 & y_2 & y_1 & y_0 \\ & x_3 & x_2 & x_1 & x_0 \\ \hline & 1 & \overline{x_0 y_3} & x_0 y_2 & x_0 y_1 & x_0 y_0 \\ & & \overline{x_1 y_3} & x_1 y_2 & x_1 y_1 & x_1 y_0 \\ & & & \overline{x_2 y_3} & x_2 y_2 & x_2 y_1 & x_2 y_0 \\ & & & & \overline{x_3 y_3} & \overline{x_3 y_2} & \overline{x_3 y_1} & \overline{x_3 y_0} \\ \hline P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0 \end{array}$$

Same hardware as for unsigned multiplication can be used.

Comparators

Compares two n -bit numbers lexicographically: from most significant to least significant

$$\begin{array}{r} A = 100111010 \\ B = 100110011 \end{array} \Rightarrow A > B$$

Inputs	outputs		
	G	E	L
$A > B$	1	0	0
$A = B$	0	1	0
$A < B$	0	0	1

Let $A = (a_{n-1} \dots a_0)$
 $B = (b_{n-1} \dots b_0)$

Define $x_i = a_i \odot b_i$ ($\overset{a_i b_i + a_i' b_i'}{\text{equivalence}}$)

Then: $A = B$ ($E = 1$) iff $\prod_{i=0}^{n-1} x_i = 1$

$$E = \prod_{i=0}^{n-1} x_i$$

There exists $a_i > b_i$ iff $a_i b_i' = 1$

Then $A > B$ ($G=1$) iff

$$a_{n-1}b'_{n-1} + x_{n-1}a_{n-2}b'_{n-2} + x_{n-1}x_{n-2}a_{n-3}b'_{n-3} + \dots + x_{n-1}x_{n-2}\dots x_1a_0b'_0$$

$$G = \sum_{i=0}^{n-1} \left(\prod_{k=0}^i x_{n-k} \right) a_{(n-1)-i} b'_{(n-1)-i}$$


where $x_n = 1$ by definition

Similarly


$$L = \sum_{i=0}^{n-1} \left(\prod_{k=0}^i x_{n-k} \right) a'_{(n-1)-i} b_{(n-1)-i}$$

 Example: 3-bit comparator

It has 6 inputs $a_0, \dots, a_2, b_0, \dots, b_2$ hence ordinary flow with truth table will have $2^6 = 64$ entries, which will be very difficult to minimize (unless Quine-McCluskey is used). Fan-in may also be a problem




 Comparators can be cascaded. It requires 3 inputs E_{in}, L_{in}, G_{in} in addition to A and B , and produces $E_{out}, L_{out}, G_{out}$. The internal Logic is enhanced to account for new inputs.



Homework: Modify comparator to account L, E, G at inputs.


Multiplexers

 


2^n AND gates for $I_0, \dots, I_{2^n-1}$

$(n+1)$ -input AND gates are AND-ing m_k and I_k

 An E (enable) is also possible for the sake of building MUX trees. E is input of any AND



 Selection is made with $S_{n-1} \dots S_0$ and E , hence selecting one of 2^{n+1} inputs




Multiplexers as Universal Logic Module

Any Boolean function of $n+1$ variables can be implemented by $2^n \times 1$ mux by assigning n variables to selection lines, say $x_0, \dots, x_{n-1}$, and $\{x_n, x_n', 0, 1\}$ to the 2^n input lines.

 
Example: $F = \sum (0, 1, 3, 6, 7, 8, 11, 12, 14)$

$$\begin{aligned}
 F &= x_1' x_2' x_3' x_4' + x_1' x_2' x_3' x_4 + x_1' x_2' x_3 x_4' + x_1' x_2 x_3 x_4' \\
 &\quad + x_1 x_2' x_3' x_4' + x_1 x_2' x_3 x_4 + x_1 x_2 x_3' x_4' + x_1 x_2 x_3 x_4' \\
 &= m_0 x_4' + m_0 x_4 + m_1 x_4 + m_3 x_4' + m_3 x_4 + m_4 x_4' \\
 &\quad + m_5 x_4 + m_6 x_4' + m_7 x_4' = \\
 &= m_0 \cdot 1 + m_1 x_4 + m_2 \cdot 0 + m_3 \cdot 1 + m_4 x_4' + \\
 &\quad m_5 x_4 + m_6 x_4' + m_7 x_4'
 \end{aligned}$$




Notice that the assignment of variables to selection lines is arbitrary

 More straight forward but less efficient
 is to use $2^n \times 1$ MUX for n -variable function
 by connecting all inputs to 0 or 1




Decoders

 Device with n inputs and $m \leq 2^n$ outputs
 whose values are mutually exclusive



 $n \times m$ decoder comprises m AND gates. If $m=2^n$ then all AND gates are of n inputs. Otherwise some AND gates may have less than n inputs.




Inputs

	x_1	x_2	$\dots$	x_n	D_0	D_1	$\dots$	D_{2^n-1}
0	0	0	$\dots$	0	1	0	$\dots$	0
1	0	1	0	$\dots$	0	1	$\dots$	0
		$\vdots$						
2^n-1	1	1	$\dots$	1	0	0	$\dots$	1




1's on diagonal
0 elsewhere

 Two m -input decoders can form $(n+1) \times 2^m$ decoding by connecting the additional variable to the enable



Decoders can implement any Boolean function by OR-ing all D_i 's corresponding to the minterms of Canonical SOP

 Decoder can be utilized as demultiplexer, connecting a single input into one of 2^n outputs as follows. ① use the n -inputs for selection ② connect the signal input to E



The inputs of decoder are used as selection lines.

Encoders

$M \leq 2^n$ inputs, n outputs. It generates the binary code of the m input variables.


Inputs must be mutually exclusive.

We then OR the input lines which result (participate) in the generation of the output code.

Example: Octal (8-lines) to Binary
($\log_2 8 = 3$ outputs) encoding

Input Data								Output Code		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x_1	x_2	x_3
1								0	0	0
	1							0	0	1
		1						0	1	0
			1					0	1	1
				1				1	0	0
					1			1	0	1
						1		1	1	0
							1	1	1	1

D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7

 

Priority Encoder 86

What happens when inputs are not mutually exclusive? This is the reality.

Example: 8 customers are requesting service. There maybe simultaneous requests. We use a priority encoder which decides that the highest index call will be served.

D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1								0	0	0
	1							0	0	1
		1					0	0	1	0
			1					0	1	1
				1				1	0	0
					1			1	0	1
						1		1	1	0
							1	1	1	1

We use the following equality

$$s + s't = \underbrace{s''s + st}_{\text{absorption}} + \underbrace{ss' + s't}_{\text{distribution}} = (s + s')(s + t) = s + t$$

87

$$x = D_4 D_5' D_6' D_7' + D_5 D_6' D_7' + D_6 D_7' + D_7$$

$$\begin{aligned}
 & \underbrace{D_4 D_5' D_6' D_7' + D_5 D_6' D_7' + D_6 D_7'}_{D_5 D_7' + D_6} + D_7 \\
 & \underbrace{D_5 D_7' + D_6}_{D_5 + D_7} + D_4 D_5' D_6' D_7' \\
 & \underbrace{D_5 + D_7}_{D_5 + D_6} + D_4 D_5' D_6' D_7' \\
 & \underbrace{D_5 + D_6}_{D_5 + D_6} + D_4 D_5' D_6' D_7'
 \end{aligned}$$

use in 4th
K-map

$$x = D_4 + D_5 + D_6 + D_7$$

Homework : prove that

$$y = D_2 D_4' D_5' + D_3 D_4' D_5' + D_6 + D_7$$

$$z = D_1 D_2' D_4' D_6' + D_3 D_4' D_6' + D_5 D_6' + D_7$$