

Asynchronous Circuit Design

Design Spec.



①

- Primitive flow table
- state Diagram




②

State Reduction



③

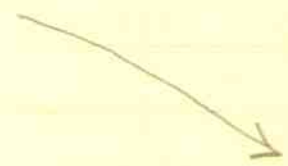- Critical Race-free state assignment
- Derive transition table



④, ⑤

- Circuit excitation table
- Latches excitation equations

- Next state equations
- Assign unspecified outputs
- Derive output equations



Circuit Logic diagram

Design Example -42-

handret A bulb A

handret B bulb B

Replaced (a) OFF

Replaced OFF

$\left. \begin{matrix} \text{Lifted} \\ \text{Replaced} \\ \text{Lifted} \\ \text{Lifted} \end{matrix} \right\} \begin{matrix} \text{(b) OFF} \\ \text{(c) ON} \\ \text{(d) OFF} \\ \text{(e) ON} \end{matrix}$

$\left. \begin{matrix} \text{Replaced} \\ \text{Lifted} \\ \text{Lifted} \\ \text{Replaced} \\ \text{Lifted} \end{matrix} \right\} \begin{matrix} \text{ON} \\ \text{OFF} \\ \text{ON} \\ \text{OFF} \\ \text{OFF} \end{matrix}$

Initially both handrets are replaced. Ignore the case of both switch state simultaneously.

x_1, x_2 - handret status 0-replaced, 1-lifted

z_1, z_2 - bulb ON, OFF

State definition for Moore Model


a - both handrets replaced ($z_1 z_2 = 00$)

b - A lifted ($z_1 z_2 = 01$) c - B lifted ($z_1 z_2 = 10$)

d - the counterpart lifted ($z_1 z_2 = 11$)

e - A replaced ($z_1 z_2 = 01$), f - B replaced ($z_1 z_2 = 10$)

Step ①

 


NS
x₁x₂

ps	00	01	11	10	outputs z ₁ z ₂
a	Ⓐ	c	—	b	00
b	a	—	d	Ⓑ	01
c	a	Ⓒ	d	—	10
d	—	e	Ⓓ	f	00
e	a	Ⓔ	d	—	01
f	a	—	d	Ⓕ	10

Step (2) simplification

 - No redundant states (homework)
- Better merging with Mealy (due to less conflict chance at outputs of stable states).



(a, b, c), (e, f, g)
Smallest cover

PS	NS/output $z_1 z_2$ Input $x_1 x_2$			
	00	01	11	10
a	(a/00)	(a/10)	b/-	(a/01)
b	a/-	(b/01)	(b/00)	(b/10)

Step (3) state assignment - trivial, no races

y	$Y/Z_1 Z_2$ $x_1 x_2$			
	00	01	11	10
0	(0/00)	(0/10)	1/-	(0/01)
1	0/-	(1/01)	(1/00)	(1/10)

Step ④ Equation derivation

Y- next state

$y \backslash x_1 x_2$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$Y = x_1 x_2 + y(x_1 + x_2)$$

Output - assignment of unspecified outputs

z_1

$x_1 x_2$	00	01	11	10
0	0	1	<u>0</u>	0
1	<u>0</u>	0	0	1

z_2

	00	01	11	10
0	0	0	<u>0</u>	1
1	<u>0</u>	1	0	0

unspecified must be set both to 0 in order

to avoid spikes of 1 at unstable states

Here is the rule:

① If the value of some output doesn't change between two stable states, it must be set the same at each unstable states through which transition occurs.


② If the value of any output does change value in transition between two stable states, it can be assigned X (don't care) at each unstable state through which transition occurs.

$$Z_1 = x_1'x_2y' + x_1x_2'y$$

$$Z_2 = x_1'x_2y + x_1x_2'y'$$

At this point fully functional circuit can be implemented where the internal signal propagation delay suffices for feedback loop delay.

-47

 

to be replaced by latches

Step ⑤ Implementation with Latches

No general procedure to determine which type of latch yields minimum logic to generate S or R . In any case, Q and Q' are used for y and y'

① The logic equation of Y was found as

$$(*) \quad Y = x_1 x_2 + y(x_1 + x_2)$$


② Characteristic equation of SR Latch is

$$Q^+ = R'Q + S \quad (SR=0)$$

Namely $(**) \quad Y = R'y + S$

Comparing $(*)$ with $(**)$ yields:
 
$$R' = x_1 + x_2 \Rightarrow R = x_1' x_2', \quad S = x_1 x_2$$




must validate
that $SR=0$

$$SR = x_1 x_2 x_1' x_2' = 0 \text{ indeed}$$

Design example

Positive Edge-Triggered Flip-Flop

 

Data is transferred to Q only on positive edge ($0 \rightarrow 1$ transition) of clock

$D=1 \Rightarrow Q=1$ on change of C from $0 \rightarrow 1$


$D=0 \Rightarrow Q=0$ -12

There are 2 inputs CD and 1 output Q

Moore model

Let us start with a state where output is either 0 or 1, hence Q


Step 1

 

Primitive state table

	CD				
	00	01	11	10	Q ⁺
a	(a)	b	-	c	Q
b	a	(b)	d	-	Q
c	a	-	f	(c)	0
d	-	b	(d)	e	1
e	a	-	d	(e)	1
f	-	b	(f)	c	0

Design implementation with SR Latch

 

We'll generate S and R from flow table to drive an active-low (NAND) latch

S	R	Q^+
1	1	Q
1	0	0
0	1	1
0	0	Indeterminate

Step ② reducing table

- No redundant states
- Merging yields (a,b), (c,f), (d,e)

A B C

-52-

PS	NS Input (CD)				Output Q+
	00	01	11	10	
A	(A)	(A)	C	B	Q
B	A	A	(B)	(B)	0
C	A	A	(C)	(C)	1

There are 3 states, hence 2 state variables,
hence 2 memory elements (2 SR latches)
state assignment $A=11, B=10, C=01$
is races-free and
corresponds to the valid inputs of SR
active-low characteristic table (00 is invalid)

PS $y_1 y_2$	NS ($Y_1 Y_2$) CD			
	00	01	11	10
11	(11)	(11)	01	10
10	11	11	(10)	(10)
01	11	11	(01)	(01)
00	X	X	X	X

y_1 and y_2
4-variable
K-map

Invalid, will never happen due to state assignment

Step (4) - Derive equations, use K-map

$$Y_1 = C' + Y_1 Y_2' + D' Y_1$$

$$Y_2 = C' + Y_1' + D Y_2$$

We can build now the circuits for Y_1 and Y_2 with internal propagation delay for memory and connect to SR latch to generate Q .


Instead, let's implement with Latches

Step (5) use latches

Active-low characteristic equation


$$Y_1 = \{C [(D Y_2)' Y_1]\}' \Rightarrow \begin{aligned} S_1 &= C \\ R_1 &= (D Y_2)' \end{aligned}$$
 
$$Y_2 = [C Y_1 (D Y_2)']' \Rightarrow \begin{aligned} S_2 &= C Y_1 \\ R_2 &= D \end{aligned}$$



When drawing, start with the building blocks alone. Then identify IO of each. Then complete all internal connections to provide proper excitations.

Example - aligning a signal to clock

 

- Input x goes to 1 only when clock C is 1
 - Input x goes to 0 only when clock C is 0
 - output is synchronized to next clock and results a pulse of one clock, regardless of the input pulse width
- System in "rest" both clock and data are 0. Output is 0
 - System gets ready to accept input Pulse as clock goes to 1. Output still 0
 - Input data changed to 1 while


clock is 1. Output still 0

d- clock pulse ended and data still 1

e- data pulse ended (went to 0) while clock was 0. System gets ready to generate pulse in sync with next clock.

f- clock arrives, a pulse is issued, output is 1.

Step ①

 

Mealy


Primitive flow table

PS	NS/output (z)			
	Input (x C)			
	00	01	11	10
a	(a/0)	b/-	-/-	-/-
b	a/-	(b/0)	c/-	-/-
c	-/-	-/-	(c/0)	d/-
d	e/-	-/-	-/-	(d/0)
e	(e/0)	f/-	-/-	-/-
f	a/-	(f/1)	-/-	-/-

Step ② - State reduction

- no equivalent states

- Merging

 


(a,b,c), (d,e), (f) ∩ (a,b), (c,d,e), (f)

(a,b), (c,f), (d,e)

PS	00	01	11	10
L	(L/0)	(L/0)	M/-	-/-
M	(M/0)	N/-	(M/0)	(M/0)
N	L/-	(N/1)	-/-	-/-

Step (3) - state assignment

 

No race-free assignment. We'll add another row with unstable state

$y_1 y_2$	00	01	11	10
00	(00/0)	(00/0)	01/-	-/-
01	(01/0)	11/-	(01/0)	(01/0)
11	10/-	(11/1)	-/-	-/-
10	00/-	-/-	-/-	-/-

Step ④ Next state and output equations

$y_1 y_2 \backslash xG$	00	01	11	10
00	0	0	0	X
01	0	1	0	0
11	1	1	X	X
10	0	X	X	X

(*) K-map for Y_1

$$Y_1 = y_1 y_2 + y_2 x'G$$

$y_1 y_2 \backslash xG$	00	01	11	10
00	0	0	1	X
01	1	1	1	1
11	0	1	X	X
10	0	X	X	X

These have been set to 1 for Y_1 . Since row is 11, they must stay 0, otherwise unwanted stable states 11 will be created

(**)
$$Y_2 = y_1' y_2 + y_2 x'G + y_1' x$$

$$= y_2 (y_1' + x'G) + y_1' x$$

$$Z = Y_1$$

Step ⑤ Implementation with latches

We'll use active-high latches

$$Q^+ = R'Q + S \quad (SR=0)$$

from (*) it follows:

$$R_1 = y_2', \quad S_1 = y_2 x'G, \quad \text{and indeed}$$

$$S_1 R_1 = y_2' y_2 x'G = 0$$

from (**) it follows

$$R_2 = (y_1' + x'G)' = y_1(x+c'), \quad S_2 = y_1'x \text{ and}$$

$$\text{indeed, } S_2 R_2 = y_1' x y_1(x+c') = 0$$