
 



Digital Logic Design

 


Out of the 16 2-Variable functions, 8 are of interest



Example

 

 

Decimal	Inputs				Outputs						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1
3											
4											
5											
6											
7											
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	1	1	1

We assume that input combinations 10, 11, ..., 15 never occur. If we complete the table, the corresponding outputs a to g are X - don't care.

We sum the minterms which turn on every segment.


$$a = \sum(0, 2, 3, 5, 7, 8, 9) = \prod(1, 4, 6)$$

$$c = \sum(0, 3, 4, 5, 6, 7, 8, 9) = \prod(1, 2)$$


$$\vdots$$

$$g = \sum(2, 3, 4, 5, 6, 8, 9) = \prod(0, 1, 7)$$

 It looks as POS is more efficient than SOP. We can implement any, using OR-AND (NOR-NOR) or AND-OR (NAND-NAND)




Example 4x1 multiplexer

 

S_1	S_0	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


I_0 is selected by 00, I_1 by 01, I_2 by 10 and I_3 by 11.
 
$$F = (S_1 + S_0 + I_0)(S_1 + S_0' + I_1)(S_1' + S_0 + I_2)(S_1' + S_0' + I_3) = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$




Combinational Logic Circuits

Combinational System

 

Outputs are fully characterized by the 2^n input combinations

Sequential System

 

Output depends on both current inputs and previous inputs, hence memory devices are required.

Combinational logic should be minimized - cost of implementation, Silicon area, power, yield

There are however delay implication.

Analysis and design of combinational circuits


- Verbal description
- Circuit logic diagram
- Boolean expressions
- truth table
- Functional description - what does it do?
- Structural description - How it does it

Design and Analysis are opposites

Analysis Procedure

- ① There must be gates whose inputs are all defined
 - ② Write output of gates in ①
 - ③ Stop, if all outputs of diagram are defined
 - ④ go to 1
- 

 
Example: circuit diagram $\rightarrow$ expression



Example: expression $\rightarrow$ circuit diagram


$$F = x_1 x_2 (x_4 + x_5) + x_3 (x_4 + x_5') + x_1 x_2 x_6' x_7 + x_3 x_6 x_7$$

Build expression tree, rooted at F

 

Each node is translated into AND or OR gate, depending on level in tree. Leaves are inputs

Design Procedure

 

Example: Binary full-adder


$$\begin{array}{r} \text{nnnn} \\ + \quad 10110 \\ \quad 11011 \\ \hline 110001 \end{array}$$

Basic operation: adding 3 bits
addend + augend + carry in
result: sum bit, carry out bit

addend x_1	augmend x_2	carry in x_3	sum S	carry out C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \sum (1, 2, 4, 7) = x_1'x_2'x_3 + x_1'x_2x_3' + x_1x_2'x_3' + x_1x_2x_3$$
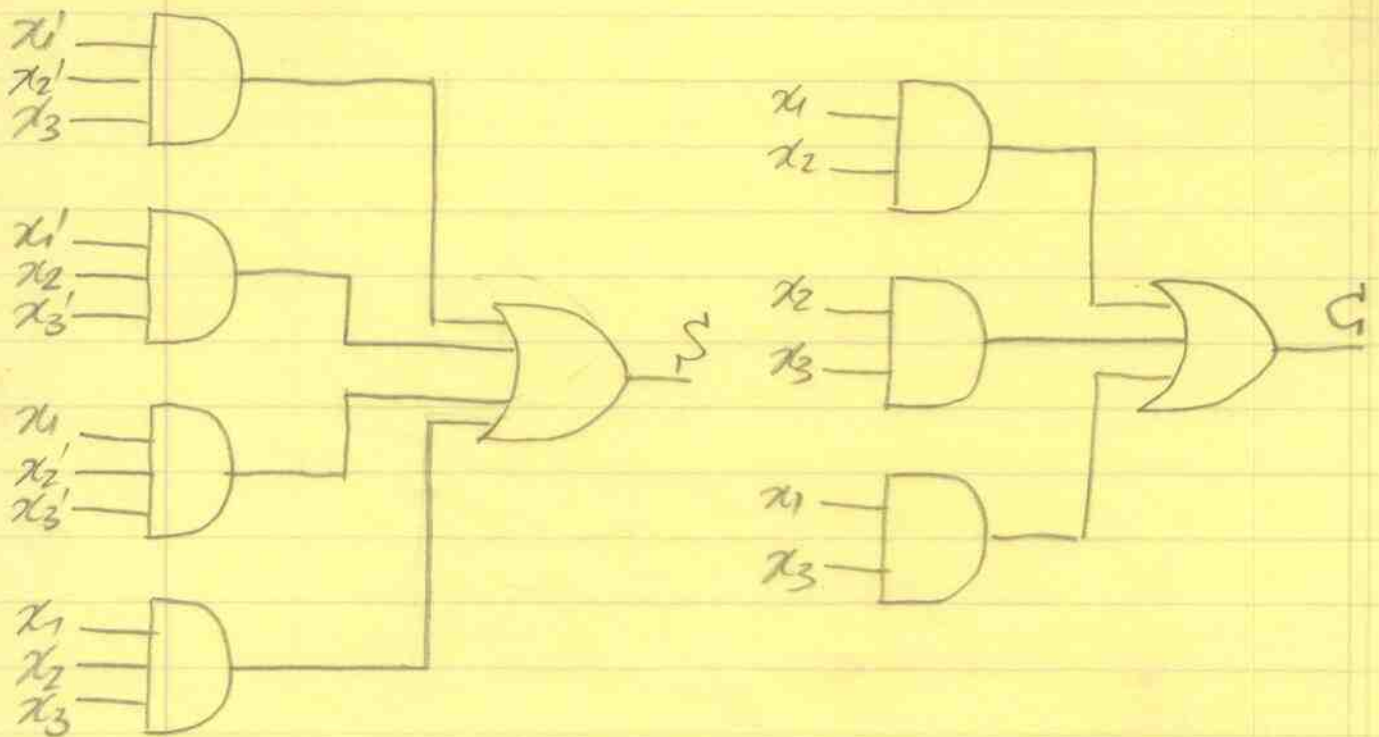
$$C = \sum (3, 5, 6, 7) = x_1'x_2x_3 + x_1x_2'x_3 + x_1x_2x_3' + x_1x_2x_3 = x_1x_2 + x_2x_3 + x_1x_3$$



Sum can be implemented as $x_1 \oplus x_2 \oplus x_3$

$$\begin{aligned} S &= x_1'x_2'x_3' + x_1'x_2x_3' + x_1x_2'x_3' + x_1x_2x_3 = \\ &= (x_1'x_2 + x_1x_2')x_3' + (x_1'x_2' + x_1x_2)x_3 \end{aligned}$$

but $(x_1'x_2' + x_1x_2)' = (x_1 + x_2)(x_1' + x_2') = x_1x_2' + x_1'x_2 =$
 $= x_1 \oplus x_2$

hence

$$S = (x_1 \oplus x_2)x_3' + (x_1 \oplus x_2)'x_3 = x_1 \oplus x_2 \oplus x_3$$

Example: Monitoring device

Electric motor supplied by 3 generators

Warning Lamp: iff 1 or 2 generators fail $L=1$


Acoustic alarm: iff 2 or 3 generators fail $A=1$

$x_i = 1$: motor i fails, $x_i = 0$ otherwise

$$L'(x_1, x_2, x_3) = x_1'x_2'x_3' + x_1x_2x_3$$

$$L(x_1, x_2, x_3) = (x_1 + x_2 + x_3)(x_1' + x_2' + x_3')$$
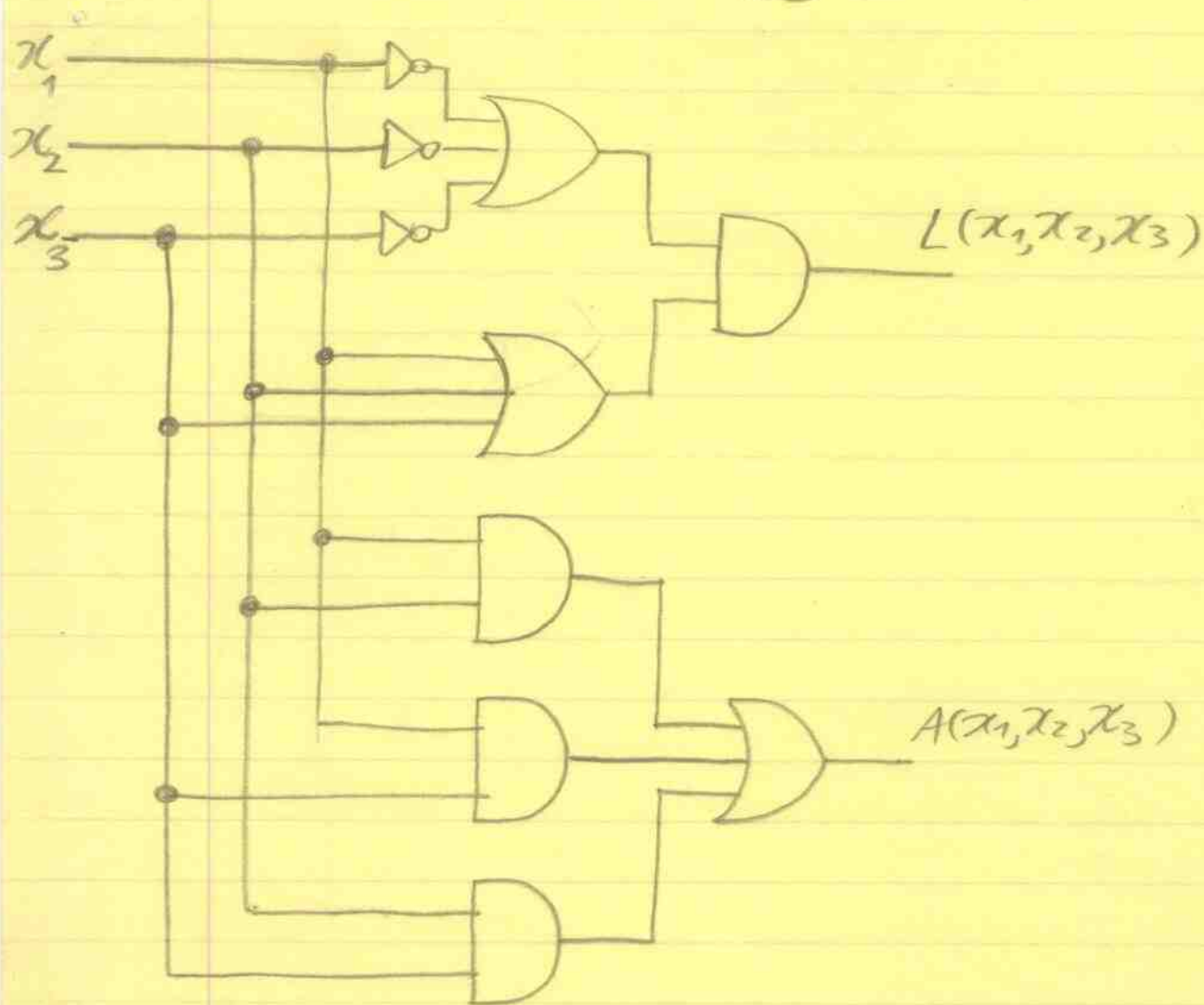
$$\begin{aligned} A(x_1, x_2, x_3) &= x_1x_2x_3' + x_1x_2'x_3 + x_1'x_2x_3 + x_1x_2x_3 = \\ &= x_1x_2 + x_2x_3 + x_1x_3 \end{aligned}$$



Logic Minimization

Combinational design problem $\rightarrow$ Boolean function

Complexity: $\# \text{ literals} \rightarrow \# \text{ transistors}$
 $\# \text{ terms} \rightarrow \# \text{ gates} + \# \text{ transistors}$

Minimize Boolean functions, redundancy removal
 redundancy and reliability

Example: $\Sigma(0, 2, 4, 5, 7) = x_1'x_3' + x_1x_2' + x_1x_3$

① ②

① 5-input OR gate + 5 3-input AND gate

② 3-input OR gate + 3 2-input AND gate

minimality 1st # terms 2nd # literals
in SOP (or POS)

Two-level circuit (SOP or POS)

- Less propagation delay
- High fan in
- Many literals

multi-level (mixed)

- more delay
- less fan in
- less literals

$$x_1'x_3'x_4 + x_1'x_2x_4 + x_2x_3x_4 = x_2x_4(x_1' + x_3) + x_1'x_3'x_4$$

2-level

7 literals


4 gates

3-level


7 literals

4 gates

 levels: maximum # gates from any input to any output



SOP

 

POS

Minimization by Boolean Algebra Theorems

Example: $F(x_1, x_2, x_3) = \sum(0, 2, 3, 4, 5, 7)$

$$= \underline{x_1'x_2'x_3'} + \underline{x_1'x_2x_3'} + \underline{x_1'x_2x_3} + \underline{x_1x_2'x_3'} + \underline{x_1x_2'x_3} + \underline{x_1x_2x_3} =$$

duplicate m_0 and m_7 and use logical adjacency

$$= x_1'x_3'(x_2' + x_2) + (x_1' + x_1)x_2'x_3' + (x_1' + x_1)x_2x_3 + x_1(x_2' + x_2)x_3 = x_1'x_3' + x_2'x_3' + x_2x_3 + x_1x_3$$

which cannot further be simplified. But different pairing m_0-m_2 , m_4-m_5 , m_3-m_7

$$F = x_1'x_3' + x_1x_2' + x_2x_3$$

Which is simpler

Example: repeated application of logical adjacency

$$F(x_1, x_2, x_3, x_4) = \sum(12, 13, 14, 15) =$$

$$= \underline{x_1x_2x_3'x_4'} + \underline{x_1x_2x_3'x_4} + \underline{x_1x_2x_3x_4'} + \underline{x_1x_2x_3x_4} =$$

$$= \underline{x_1x_2x_3'}(x_4' + x_4) + \underline{x_1x_2x_3}(x_4' + x_4) = \underline{x_1x_2}(x_3' + x_3)$$

$$= x_1x_2$$

Theorem: Let $F(x_0, \dots, x_{n-1})$ be expressed by a sum of 2^m minterms, $m \leq n$. Let $m-m$ variables be identical in all minterms. Then F can be simplified into single product of the $n-m$ variables.

Proof: By induction on m - the number of non identical variables. Assume that there are $x_0, \dots, x_{m-1}$.

There are 2^m distinct products of $x_0, \dots, x_{m-1}$, hence they span all minterms.

2^{m-1} of which have x_0 literal and 2^{m-1} have x_0' . Therefore

$$F = x_0 \sum_1 (\quad) + x_0' \sum_2 (\quad).$$

The induction hypothesis holds for $\sum_1$ and $\sum_2$ which can be simplified into product term of $n-m$ variables. But these products are identical.
 $(n-2) - (m-1) = n-m$

Now we apply the rule of logical adjacency and the theorem follows.

We need more systematic way for simplifying Boolean Functions