


Sequential circuit that follows a sequence of distinct states under the control of input clock pulses.

Ripple counters Vs. Synchronous counters
up counter, down counter

Modulo-M counter counts up to M pulses

Natural modulus counter counts $M=2^N$ pulses and requires $N=\log_2 M$ FF's for implementation, known as N-bit counter.

 Example - Mod-8 counter - Synchronous since pulses are entered to CLK inputs of all FF's



States can be stored in negative edge-triggered T FF's

in Negative edge TFF clock is entered with negation

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0


Excitation Table

PS	y_2	y_1	y_0	NS	Y_2	Y_1	Y_0	T_2	T_1	T_0
S_0	0	0	0	S_1	0	0	1	0	0	1
S_1	0	0	1	S_2	0	1	0	0	1	1
S_2	0	1	0	S_3	0	1	1	0	0	1
S_3	0	1	1	S_4	1	0	0	1	1	1
S_4	1	0	0	S_5	1	0	1	0	0	1
S_5	1	0	1	S_6	1	1	0	0	1	1
S_6	1	1	0	S_7	1	1	1	0	0	1
S_7	1	1	1	S_0	0	0	0	1	1	1


With the aid of K-map ($y_2 y_1 y_0$) we obtain

$$T_2 = y_1 y_0 \quad T_1 = y_0 \quad T_0 = 1$$

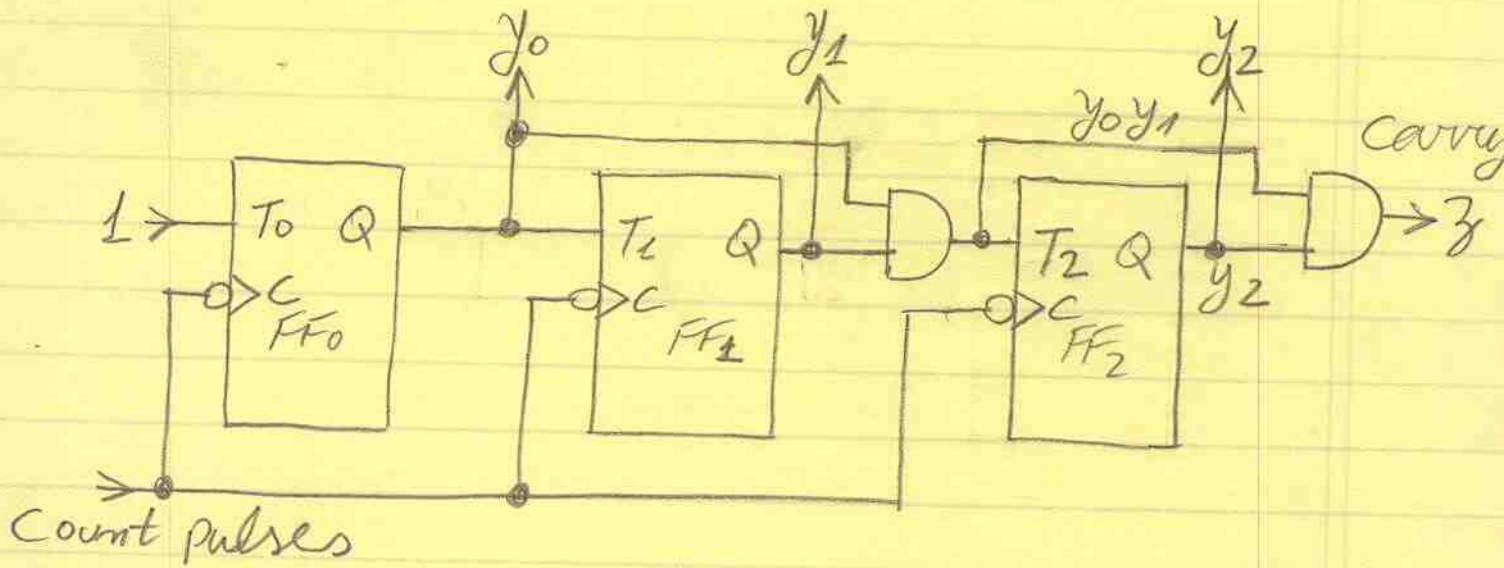$z = y_1 y_2 y_3$ - Indication on 8 counts



Implementing Mod-M/K counter

 

-21-

Example: decimal counter with JK FF's

- We use BCD state assignment

$Q(t)$	$Q(t+1)$	J	K	excitation table
0	0	0	X	
0	1	1	X	
1	0	X	1	
1	1	X	0	


PS				NS				$J_3 K_3 \dots J_0 K_0$
y_3	y_2	y_1	y_0	Y_3	Y_2	Y_1	Y_0	
0	0	0	0	0	0	0	1	
0	0	0	1	0	0	1	0	
0	0	1	0	0	0	1	1	
0	0	1	1	0	1	0	0	
0	1	0	0	0	1	0	1	
0	1	0	1	0	1	1	0	
0	1	1	0	0	1	1	1	
0	1	1	1	1	0	0	0	
1	0	0	0	1	0	0	1	
1	0	0	1	0	0	0	0	

We create now a table of $J_i K_i$ by replacing the Y_i with their corresponding implied JK excitation values.

For instance, $(y_0, Y_0) = (0, 1)$ results
 $(J_0, K_0) = (1, X)$, or $(y_3, Y_3) = (1, 0)$ results
 $(J_3, K_3) = (X, 1)$. We then obtain the
table for all J_i and K_i

y_3	y_2	y_1	y_0	J_3	K_3	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	0	0	X	0	X	0	X	1	X
		$\vdots$					$\vdots$				
1	0	0	1	X	1	0	X	0	X	X	1

 And then every J_i and K_i equation is obtained
by K-map



$$J_0 = K_0 = 1$$

$$J_1 = y_3' y_0, \quad K_1 = y_0$$


$$J_2 = K_2 = y_1 y_0$$

$$Z = y_3 y_0$$

$$J_3 = y_2 y_1 y_0, \quad K_3 = y_0$$


Important: Need to check whether this is self-starting state ^{code} assignment.

- ① We need to set $y_3 y_2 y_1 y_0$ all unused codes (circuit can start with arbitrary values of y_i 's)
- ② For each unused code calculate all J_i and K_i to find Y_i $i=0,1,2,3$ and then derive $Y_3 Y_2 Y_1 Y_0$
- ③ If $Y_3 Y_2 Y_1 Y_0$ correspond to any assigned code we are done. Otherwise process repeats. If none reach to a state code then state assignment needs take all codes and create transition to defined states.

 


1100 → 1101 → 0100 used code


1110 → 1111 → 0000 used code

 


Ripple Counters

 

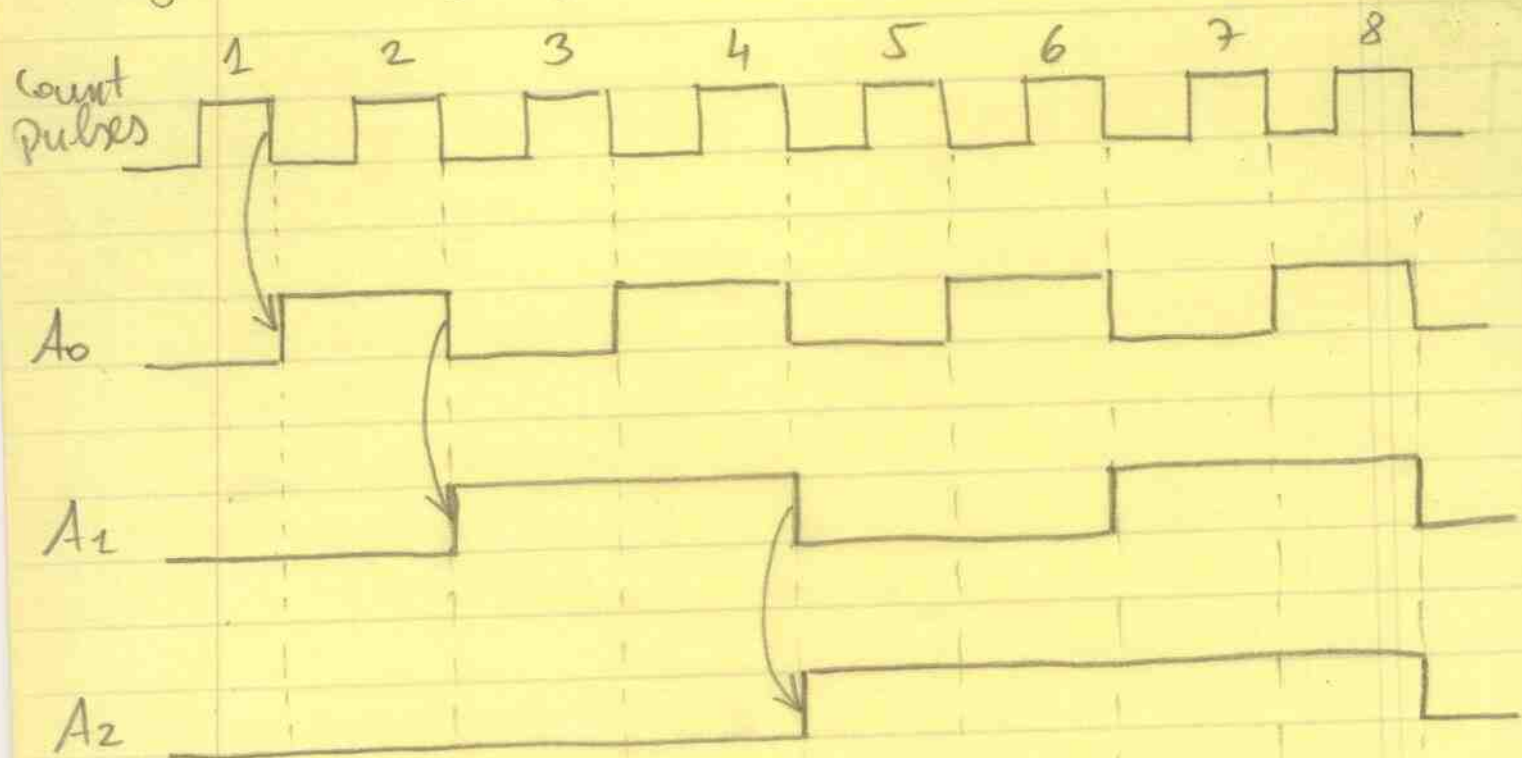Counter is cleared (asynchronously), all A's 0
 All J's and K's are permanently 1, so any
 negative edge of clock will complement Q



 - This is called **mod-M** ($M=8$) counter and also **divide-by-M** counter
- This is an **up-counter**, counting from 0 to 7. Looking at Q' it is a **down-counter**
- Here is a ripple **up/down** counter



when $U/D=1$ it is up-counter



when $U/D=0$ it is down-counter

Ripple Counters with arbitrary modulus

The idea is to generate a **clear (reset)**

pulse upon the occurrence of M at $A_0 A_1 \dots$

which will then reset the counter

 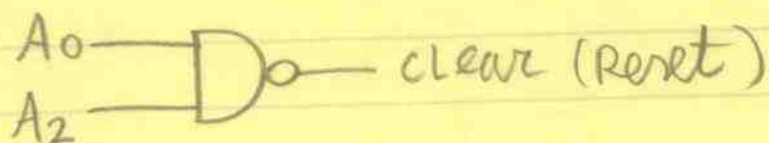

spike may be a problem. Its width is defined by internal delays, which limit frequency of pulses.

Also, if $A_0 A_1 A_2$ is used, A_0 's spike may be a problem

conditions of clear to change from 1 to 0


occur at 5th pulse falling edge, where

$A_0 A_1 A_2 = 101$, $CLEAR = 0$ which then resets


$A_0 A_1 A_2 = 000$ AND $CLEAR = 1$

Selectable Modulo Counter

 An N -bit counter can be "programmed" to any $M \leq 2^N$ modulus as follows



Presettable Counters

 

Sometimes we'd like an M -counter to count up from K to M or down from M to K , $0 \leq K \leq M-1$. This is accomplished by parallel load of K to the preset asynchronous input of the FF. Let $K = I_2 I_1 I_0$, $I_i = 0, 1$. Once $LOAD = 1$, preset inputs will receive 0, while clear input = 1, hence $Q_i = 1$. If $I_i = 0$, preset = 1 and clear = 0, hence $Q_i = 0$ at presetting time count pulses are inhibited when $Load = 0$, counter is operating, starting count from $I_2 I_1 I_0$.

Propagation delay in ripple counters

Ripple counters are simple to construct but suffer from propagation delay proportional

to their size. Recall that most significant bit switches on negative edge of all other FF's, but FF_i switches only after FF_{i-1} . Therefore, the minimum time interval between successive pulses is

$$T_c \geq N \cdot t_p$$

In today's VLSI technologies $t_p = 100 \text{ pSec} = 0.1 \text{ nSec} = 10^{-10} \text{ Sec}$. Assume 4-bit counter


$$f_{\max} = \frac{1}{T_c} = \frac{1}{10^{-10} \times 4} = 2.5 \text{ GHz}$$


Synchronous Counters

Ripple counters suffer from speed of operation (propagation delay) and forced binary count sequence resulting from its construction. Any different counting sequence requires code conversion.


In synchronous counters pulses are connected to clock inputs of all FF's, allowing much faster operation. They are built similarly to ripple counters and can be configured similarly.

Special type are Ring Counters

 

 

 FF_0 is initially loaded with 1 (by **preset**) and $A_1 A_2 = 00$ (**cleared**). Hence initial state of this ring counter is 001. It will go then to 010 and 100



Not all initial FF states are **valid**,
for instance




Presetting all FF's to 1 will make 111 permanent. Clearing all to 0 will make 000 permanent. An N -bit ring counter has N valid states (incorporating single 1 and $N-1$ 0's) and $2^N - N$ invalid states.

In Order to make a ring-counter self starting. The idea is to ensure that as long as there's at least one 1's in the pipe upto A_N , A_0 sets to 0 until all pipe is 0 and then the A_0 goes to 1. This is accomplished by connecting J_0 to $(A_0 + A_1 + \dots + A_N)$.

Twisted Ring counter (Johnson, switch tail)

 The number of valid states can be doubled by connecting A_{N-1} (head of ring counter - complement) to tail J_0



Initially **CLEAR** resets all FF's then every negative **CLK** edge makes A_0 1 and pushes all 1's to next FF's until the pipe is Filled. Once A_{N-1} is 1, A_0 turns to 0 and same 0 propagation occurs for next N clock's negative edges.

1	CLEAR	0	0	0
2		1	0	0
3		1	→ 1	0
4		1	→ 1	→ 1
5		0	→ 1	→ 1
6		0	→ 0	→ 1
0		0	→ 0	→ 0
			⋮	

There are 2^N Valid states and $2^N - 2^N$ invalid ones.

Self starting is possible.

2^N is always even, but modifying to odd is possible.

Ripple counter requires decoding, Ring doesn't.

Application - Digital clock (frequency division)

- Use the 50 Hz line voltage to generate 50 Hz Pulses

- Divide by 50 With a counter to generate

1 Hz Pulses (seconds)


- Divide by 60 to generate minute pulses

- " " 60 " hours

- " " 24 to generate a day pulses

Use the output of 24-hour counter to display hours and similarly for minutes and seconds.

Application - Frequency measurement

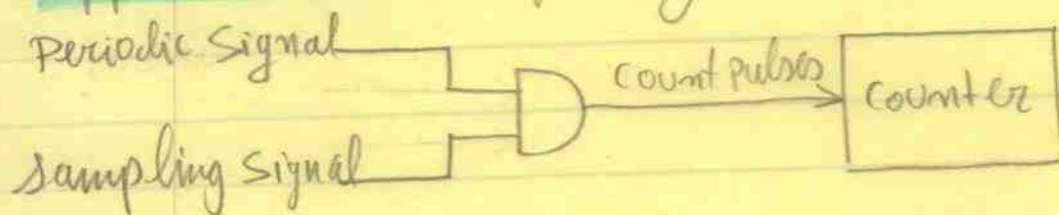

$$f = \frac{\text{Count Pulses}}{\text{Sampling time}}$$

longer sampling -
more accurate

Application - Generation of timing signals

The operation of digital systems requires various timing signals.

With N -bit binary counter we can generate any $L \leq 2^N$ timing signals as follows

