

## State Reduction

States may carry information that is found in other states. Such states are **redundant** and will be eliminated by **state reduction** procedure. This is of interest since it may reduce the number of memory devices and simplify the combinational logic implementation.

### Reduction of Completely Specified State Table

**Definition**: Two states  $s_i$  and  $s_j$  are **equivalent**,  $s_i = s_j$ , if any sequence of inputs starting at  $s_i$  results in a sequence of outputs identical to the sequence of outputs obtained by starting at  $s_j$ .

States  $s_1, s_2, \dots, s_n$  are equivalent iff they result identical output sequences for any

input sequence

State equivalence is equivalence relation

- $s_i = s_i$  for any state - reflexivity
- $s_i = s_j \iff s_j = s_i$  - symmetry
- $s_i = s_j, s_j = s_k \Rightarrow s_i = s_k$  - transitivity

State equivalence partition state set into equivalent classes, of which one state per class suffice and all the rest can be dropped.

There's no need to check all sequences of inputs!

**Theorem:** Two states  $s_i$  and  $s_j$  of a completely specified state table are equivalent iff for every input

- 1- the outputs produced by  $s_i$  and  $s_j$  are identical
- 2- next states are equivalent

**Proof:** Homework

## State equivalence implication

Let  $s_i$  and  $s_j$  have identical outputs for all inputs and identical next state for all inputs, except one input where their next-states are  $s_m$  and  $s_n$ , respectively.

It follows that  $s_i = s_j$  if  $s_m = s_n$ . We say that  $(s_i, s_j)$  implies  $(s_m, s_n)$ . It also  $(s_m, s_n)$  implies  $(s_i, s_j)$  then  $s_i = s_j$  and  $s_m = s_n$ .

### Example:

| PS   |   | NS/output |       |
|------|---|-----------|-------|
|      |   | $x=0$     | $x=1$ |
| * {  | a | c/0       | b/1   |
|      | b | d/0       | b/1   |
| ** { | c | a/1       | d/0   |
|      | d | b/1       | c/0   |

trivially true

\*  $a=b$  if  $c=d$  and  $b=b$

$(a,b)$  implies  $(c,d)$

true by symmetry  
-20-

\*\*  $(c=d)$  if  $a=b$  and  $d=c$

$(c,d)$  implies  $(a,b)$

consequently  $a=b$  and  $c=d$ . We choose  
representative state for every equivalent class,  
delete the rest rows and replace states by  
their representative.

| PS | NS/output |       |
|----|-----------|-------|
|    | $x=0$     | $x=1$ |
| a  | d/0       | a/1   |
| d  | a/1       | d/0   |

### Implication Table

| PS | NS/output |       |
|----|-----------|-------|
|    | $x=0$     | $x=1$ |
| a  | b/1       | h/1   |
| b  | f/1       | d/1   |
| c  | d/0       | e/1   |
| d  | c/0       | f/1   |
| e  | d/1       | c/1   |
| f  | c/1       | c/1   |
| g  | c/1       | d/1   |
| h  | c/0       | a/1   |

Implication table is a cross reference of states (lower diagonal triangle of a matrix)

|   |                |                |                |       |       |       |   |
|---|----------------|----------------|----------------|-------|-------|-------|---|
| b | (b,f)<br>(c,h) |                |                |       |       |       |   |
| c | x              | x              |                |       |       |       |   |
| d | x              | x              | (c,d)<br>(e,f) |       |       |       |   |
| e | (b,d)<br>(c,h) | (d,f)<br>(c,d) | x              | x     |       |       |   |
| f | (b,c)<br>(c,h) | (c,f)<br>(c,d) | x              | x     | (c,d) |       |   |
| g | (b,c)<br>(c,h) | (c,f)          | x              | x     | (c,d) | (c,d) |   |
| h | x              | x              | (c,d)<br>(a,e) | (a,f) | x     | x     | x |
|   | a              | b              | c              | d     | e     | f     | g |

$(e,f)$  implies  $(c,d)$  and  $(c,d)$  implies  $(e,f)$ ,  
therefore  $e=f$  and  $c=d$ .

$(f,g)$  implies  $(c,d)$  but  $c=d$ , hence  $f=g$ .

$(e,g)$  implies  $(c,d)$ , hence  $e=g$ .

$c \neq f$ , hence  $f \neq b$  and  $g \neq b$  and  $e \neq b$

But then  $b \neq a$

$b \neq d$ , hence  $e \neq a$

$b \neq c$ , hence  $f \neq a$  and  $g \neq a$

And so on, until all entries are either  $\checkmark$  or  $\times$ .

In conclusion, we obtained the following equivalent classes

$\{a\}$ ,  $\{b\}$ ,  $\{c, d\}$ ,  $\{e, f, g\}$ ,  $\{h\}$   
 $A$        $B$        $C$        $D$        $E$


Assigning new symbols, we obtained reduced state table

| PS | NS/output |       |
|----|-----------|-------|
|    | $x=0$     | $x=1$ |
| A  | B/1       | E/1   |
| B  | D/1       | C/1   |
| C  | C/0       | D/1   |
| D  | C/1       | C/1   |
| E  | C/0       | A/1   |

# Implication graph

Vertices are states, equivalence are edges

Equivalent classes are cliques.

 

## Reduction of Flow Tables (Primitive)

| PS | NS/Output (z <sub>1</sub> z <sub>2</sub> ) |      |      |      |
|----|--------------------------------------------|------|------|------|
|    | 00                                         | 01   | 11   | 10   |
| a  | a/00                                       | b/-  | -/-  | e/-  |
| b  | c/-                                        | b/10 | f/-  | -/-  |
| c  | c/00                                       | h/-  | -/-  | d/-  |
| d  | a/-                                        | -/-  | f/-  | d/11 |
| e  | g/-                                        | -/-  | f/-  | e/11 |
| f  | -/-                                        | h/-  | f/01 | e/-  |
| g  | g/00                                       | h/-  | -/-  | e/-  |
| h  | c/-                                        | h/10 | i/-  | -/-  |
| i  | -/-                                        | j/-  | i/01 | e/-  |
| j  | a/-                                        | j/-  | i/-  | -/-  |


fundamental mode transitions are defined only for one change of one input variable

Two steps:

1- Redundant state removal as for completely specified tables


2- Row merging where few rows are captured in a single row (this is not redundancy removal)

|   |            |            |     |     |   |     |   |     |   |
|---|------------|------------|-----|-----|---|-----|---|-----|---|
| b | X          |            |     |     |   |     |   |     |   |
| c | b,h<br>d,e | X          |     |     |   |     |   |     |   |
| d | X          | X          | X   |     |   |     |   |     |   |
| e | X          | X          | X   | a,g |   |     |   |     |   |
| f | X          | X          | X   | X   | X |     |   |     |   |
| g | b,h        | X          | d,e | X   | X | X   |   |     |   |
| h | X          | f,i        | X   | X   | X | X   | X |     |   |
| i | X          | X          | X   | X   | X | h,j | X | X   |   |
| j | X          | a,c<br>f,i | X   | X   | X | X   | X | c,a | X |
|   | a          | b          | c   | d   | e | f   | g | h   | i |

 

Consequently:
 
$$\begin{array}{ll}
 a=c=g & f=i \\
 b=h=j & d=e
 \end{array}$$



$\{a, c, g\}$ ,  $\{b, h, i\}$ ,  $\{d, e\}$ ,  $\{f, j\}$   
 $\overset{A}{\underset{A}{\parallel}}$   $\overset{B}{\underset{B}{\parallel}}$   $\overset{C}{\underset{C}{\parallel}}$   $\overset{D}{\underset{D}{\parallel}}$

| PS | NS/output ( $z_1 z_2$ ) |             |             |             |
|----|-------------------------|-------------|-------------|-------------|
|    | Input ( $x_1 x_2$ )     |             |             |             |
|    | 00                      | 01          | 11          | 10          |
| A  | <u>A/00</u>             | B/-         | -/-         | C/-         |
| B  | A/-                     | <u>B/10</u> | D/-         | -/-         |
| C  | A/-                     | -/-         | D/-         | <u>C/11</u> |
| D  | -/-                     | B/-         | <u>D/01</u> | C/-         |

## Merge Process

| PS | 00          | 01          | 11  | 10  |
|----|-------------|-------------|-----|-----|
| A  | <u>A/00</u> | B/-         | -/- | C/- |
| B  | A/-         | <u>B/10</u> | D/- | -/- |



A, B | A/00 B/10 D/- C/-

Merging C and D yields:

C, D | A/- B/- D/01 C/11

But then A, B can be merged with CD,  
Yielding

A, B, C, D | A/00 B/10 D/01 C/11

But the above has one state, thus a  
combinational logic!

Merging is valid only in fundamental-mode  
(only one input change at a time)

**Definition:** Any two rows  $r_i$  and  $r_j$  in a flow table can be merged into a single row  $(r_i, r_j)$  iff there are no conflict in any column.

Merge is not transitive

Example:

| PS | 00  | 01  | 11 | 10  |
|----|-----|-----|----|-----|
| a  | (a) | b   | -  | c   |
| b  | a   | (b) | d  | -   |
| c  | a   | -   | e  | (c) |

$(a, b)$  mergable,  $(a, c)$  mergeable but  $(c, b)$  does not!

**Definition:** Rows  $r_1, \dots, r_j$  can be merged into a single row  $(r_1, \dots, r_j)$  if any pair can be merged

# Example:

| PS | NS<br>Input ( $x_1 x_2$ ) |     |     |     | output (z) |
|----|---------------------------|-----|-----|-----|------------|
|    | 00                        | 01  | 11  | 10  |            |
| a  | (a)                       | b   | -   | f   | 0          |
| b  | a                         | (b) | d   | -   | 0          |
| c  | (c)                       | b   | -   | -   | 0          |
| d  | -                         | b   | (d) | e   | 1          |
| e  | c                         | -   | d   | (e) | 1          |
| f  | a                         | -   | d   | (f) | 0          |


Assume Moore model. Then output is associated with the entire NS of a row. Hence it must not conflict for rows subjected to merging. Hence merging results in

(a, b, f), (c), (d, e)  
A B C

2 memory elements

| PS | 00  | 01  | 11  | 10  | output (z) |
|----|-----|-----|-----|-----|------------|
| A  | (A) | (A) | C   | (A) | 0          |
| B  | (B) | A   | -   | -   | 0          |
| C  | B   | A   | (C) | (C) | 1          |

 In Mealy models outputs are associated to stable states only. Merges therefore may yield smaller table.



Minimal cardinality cover is  $(a, b, f)$ ,  $(c, d, e)$   
A B

| PS | 00    | 01    | 10    | 11    |
|----|-------|-------|-------|-------|
| A  | $A/0$ | $A/0$ | $B/-$ | $A/0$ |
| B  | $B/0$ | $A/-$ | $B/1$ | $B/1$ |

Notice the different outputs in a row. 1 memory element

## State Assignment

Assign unique binary code to states.

$n$  states require at least  $N$  state variables

$N \geq \lceil \log_2 n \rceil$ . For synchronous machines this is sufficient. Asynchronous however are more delicate due to races, and more memory devices may be required, depending on state transitions.

There are  $P = 2^N! / (2^N - n)!$

$n=4, N=2 \Rightarrow P=24, n=5, N=3 \Rightarrow P=6720$

Two different assignments may result significant hardware difference.

Two assignments are equivalent if they can be obtained from each other by complement or state variable swapping

$$(2^n)! / 2^n$$

There are therefore  $R = (2^n - 1)! / [(2^n - n)! \cdot n!]$   
different assignments  $N \uparrow \frac{n!}{n! \cdot 2^n}$


$$n=4, N=2 \Rightarrow R=3, \quad n=5, N=3 \Rightarrow R=140$$

No efficient and simple method for optimal assignment. We'll focus on robustness (race-free), although assignments resulting non-critical races are valid. Avoid state transitions that result change in more than one state variable

Example

| PS | $x_1 x_2$ |     |     |     |
|----|-----------|-----|-----|-----|
|    | 00        | 01  | 11  | 10  |
| A  | (A)       | B   | C   | (A) |
| B  | A         | (B) | (B) | C   |
| C  | B         | (C) | (C) | (C) |


Flow-table

 

State-assignment graph

State assignment graph: Vertices are states, edges are transitions.

 adjacent vertices must be assigned with 1-bit different codes. Not always possible.




**Resolution** by cycles: a sequence of unstable states that terminate in a stable state.

OR new states

We can use unspecified next states without increasing # state variables (preferred) OR using more state variable


| PS         | 00  | 01  | 11  | 10  |
|------------|-----|-----|-----|-----|
| A          | (A) | B   | D   | (A) |
| B          | A   | (B) | (B) | C   |
| C          | B   | (C) | (C) | (C) |
| new<br>→ D | -   | -   | C   | -   |

 

We broke the transition (edge in graph) between A and C by introducing new unstable state D

Example: use unspecified next states


|   | 00  | 01  | 11  | 10  |
|---|-----|-----|-----|-----|
| A | (A) | B   | C-  | C   |
| B | (B) | (B) | AC  | D   |
| C | A-  | D   | (C) | (C) |
| D | CA  | (D) | (D) | (D) |

 

Break A-D edge (due to 00 input) by replacing unstable A by C and setting unspecified to A. similar with B-C

## Adding state variables

|   | 00  | 01  | 11  | 10  |
|---|-----|-----|-----|-----|
| a | b   | (a) | (a) | b   |
| b | (b) | d   | c   | (b) |
| c | (c) | a   | (c) | d   |
| d | c   | (d) | a   | (d) |

 


addition of one state variable is a must  
to assign adjacent codes to adjacent states  
We'll have then 3 state variables

| $y_2 y_1$ | 00  | 01 | 11  | 10  |
|-----------|-----|----|-----|-----|
| 0         | a   | b  | c   | (g) |
| 1         | (e) | d  | (f) |     |


The idea is to create "path" between  
any states through new unstable state.  
This creates three new states e, f and g

-35-

|   | 00             | 01             | 11             | 10             |
|---|----------------|----------------|----------------|----------------|
| a | b              | a              | a              | b              |
| b | b              | d              | c              | b              |
| c | c              | <del>x</del> g | c              | <del>d</del> f |
| d | <del>x</del> f | d              | <del>x</del> e | d              |
| g | -              | a              | -              | -              |
| e | -              | -              | a              | -              |
| f | c              | -              | -              | d              |

 

 Any 8-row flow table that needs  
4 state variables can use the following  
template




## Memory Devices

A **latch** is a bistable device. It has output  $Q$  and its complement  $Q'$  and can be in either of  $Q=1, Q'=0$  called **set state**, or  $Q=0, Q'=1$  called **reset state**. A latch changes value when its inputs change value. Output is changed after some internal propagation delay, a property called **transparency**, common to all latches.


Flip-Flop state changes are controlled by clock input, and can change state only in response to a transition of clock signal.

## SR (Set-Reset) Latch

 

$S=0$   $R=0$  in normal operation one input changes to 1.

Active-High

 

$S=1$   $R=1$  in normal operation one input changes to 0.

Active-Low

called  $S'R'$  ( $\bar{S}-\bar{R}$ ) latch

| S | R | Q(P.S) | Q <sup>+</sup> (N.S) |
|---|---|--------|----------------------|
| 0 | 0 | 0      | 0                    |
| 0 | 0 | 1      | 1                    |
| 0 | 1 | 0      | 0                    |
| 0 | 1 | 1      | 0                    |
| 1 | 0 | 0      | 1                    |
| 1 | 0 | 1      | 1                    |
| 1 | 1 | 0      | 0                    |
| 1 | 1 | 1      | 1                    |

not  
change

Reset

Set


⇒

SR=0

| S | R | Q <sup>+</sup>         |
|---|---|------------------------|
| 0 | 0 | Q                      |
| 0 | 1 | 0                      |
| 1 | 0 | 1                      |
| 1 | 1 | nd<br>deter-<br>minate |

Characteristic table

Equivalent  
Characteristic table

 

$$Q^+ = R'Q + R'S \quad \downarrow \text{SR=0}$$

$$= R'Q + S$$

Active High

Derive excitation table: What should be S and R in order to obtain Q and Q<sup>+</sup>. It is derived from the characteristic table.


| $Q$ | $Q^+$ | $S$ | $R$ |
|-----|-------|-----|-----|
| 0   | 0     | 0   | X   |
| 0   | 1     | 1   | 0   |
| 1   | 0     | 0   | 1   |
| 1   | 1     | X   | 0   |

## Excitation table

Excitation table is useful for deriving the logic for setting  $S$  and  $R$

**D Latch** one input

 Obtained from SR latch by enforcing  $S = R'$



| $D$ | $Q^+$ |
|-----|-------|
| 0   | 0     |
| 1   | 1     |

equivalent characteristic table

$$Q^+ = D$$

| $Q$ | $Q^+$ | $D$ |
|-----|-------|-----|
| 0   | 0     | 0   |
| 0   | 1     | 1   |
| 1   | 0     | 0   |
| 1   | 1     | 1   |

Excitation table

# Gated Latches

Using enable input to control operation. Latch can change state only at  $E=1$

