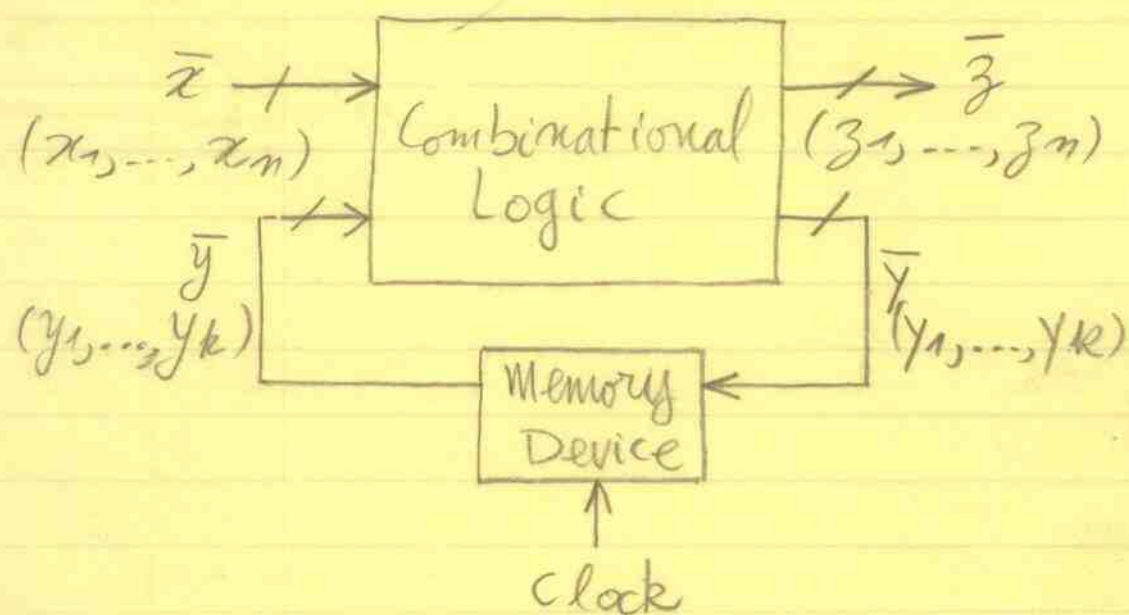


Synchronous Sequential Circuits



Clock pulses mark all delay effects

$$Y_i(t+1) = G_i(\bar{x}(t), \bar{y}(t)) \quad i=1, 2, \dots, k$$

$$Z_i(t) = F_i(\bar{x}(t), \bar{y}(t)) \quad i=1, 2, \dots, m \quad \text{Mealy}$$

$$Z_i(t) = F_i(\bar{y}(t)), \quad i=1, 2, \dots, m \quad \text{Moore}$$

t and $t+1$ are two consecutive clock pulses.


While Latches are transparent, FlipFlops are bistable devices gated by clocks.

SR FlipFlop - edge triggered

Works similar to gated SR Latch, where enable is clock (Positive edge triggered) or clock' (negative edge triggered)



positive edge triggered

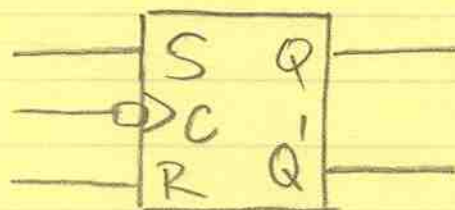

negative edge triggered



$$Q(t+1) = R'Q(t) + S \quad SR=0$$

S	R	$Q(t+1)$	$Q(t)$	$Q(t+1)$	S	R
0	0	$Q(t)$	0	0	0	X
0	1	0	0	1	1	0
1	0	1	1	0	0	1
1	1	not valid	1	1	X	0

reduced characteristic table

Excitation table

D Flip Flop - edge triggered

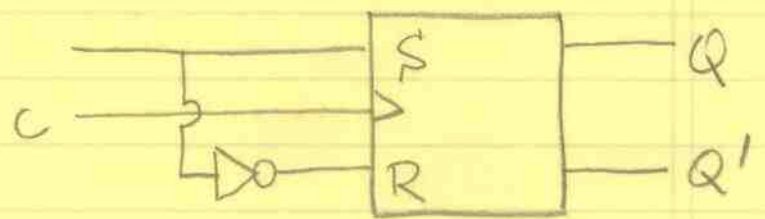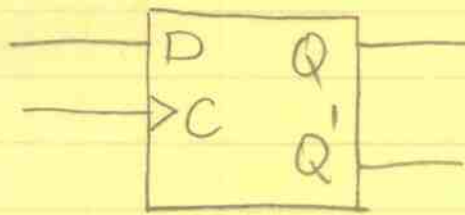

Implementation



D	$Q(t+1)$
0	0
1	1

reduced characteristic table

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation table

JK Flip Flop - edge triggered

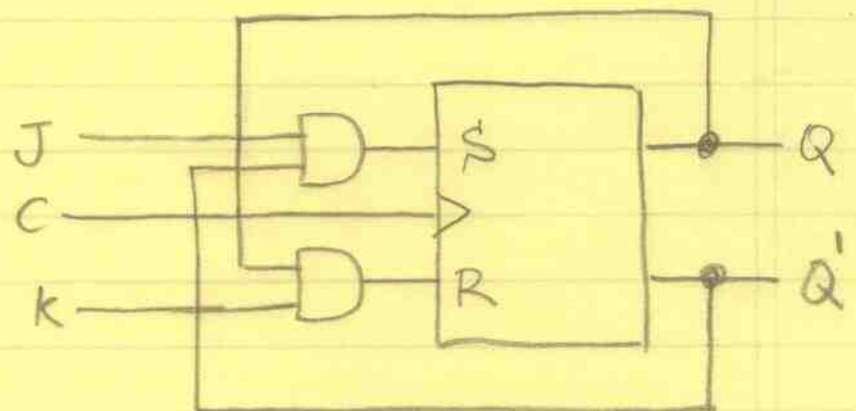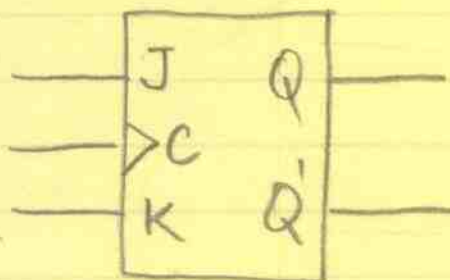

Implementation

(Unlike pure SR,)

JK output is determined for $J=1$ $K=1$

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



Reduced characteristic table

Excitation table

$$Q(t+1) = K'Q + JQ'$$

T Flip Flop - edge triggered

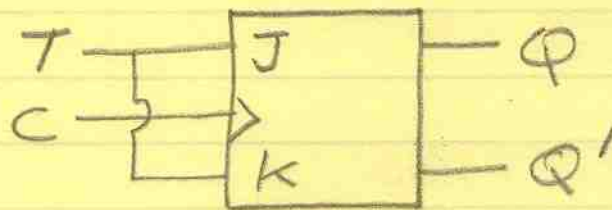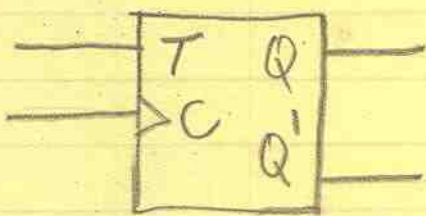Obtained from JK FF by connecting J and K




T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

characteristic table

excitation table

Analysis Example

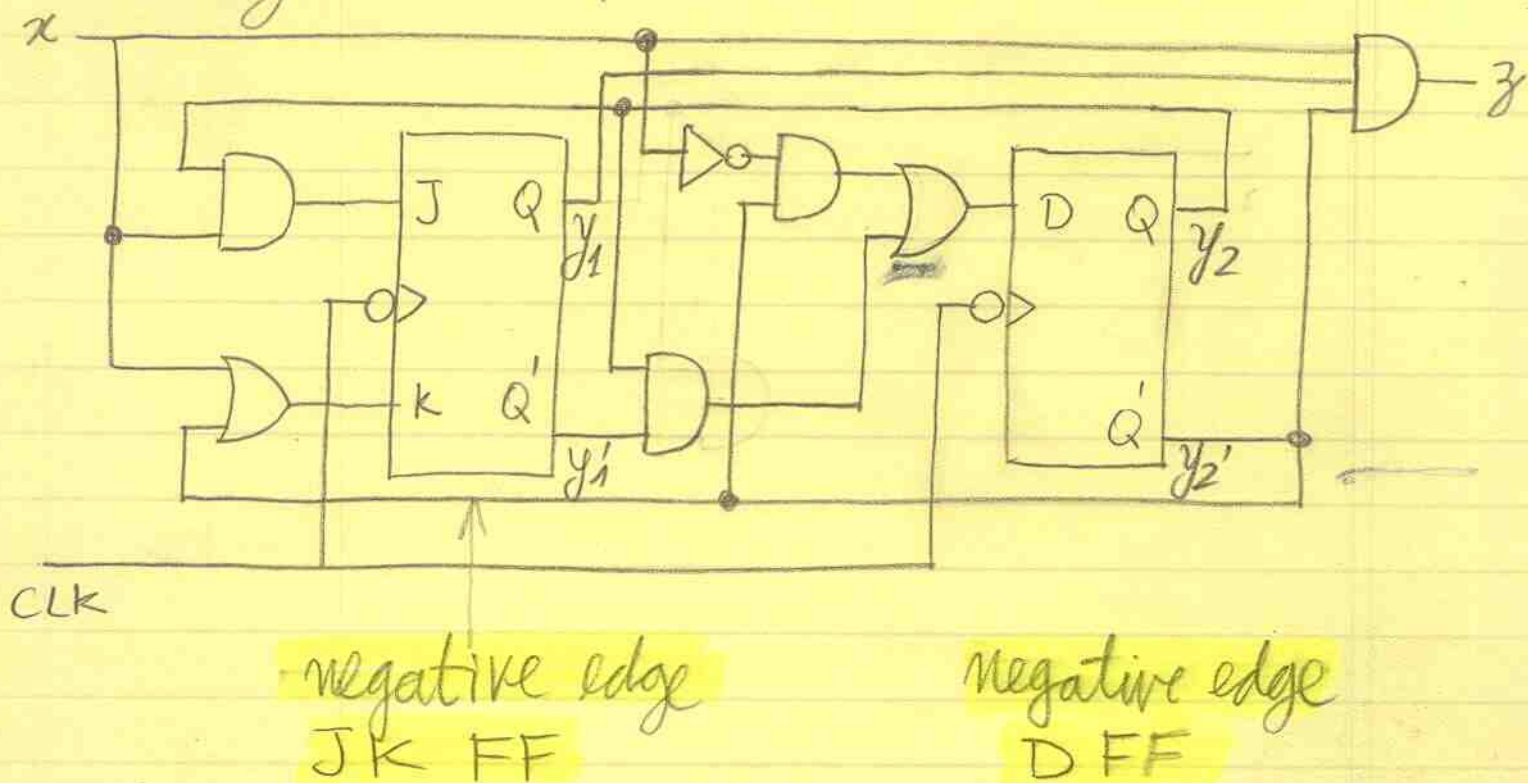

above circuit has $y_1 y_2$ states variables, hence there are 4 states 00 01 11 and 10

Excitation equations

$$J = x y_2$$

$$K = x + y_2'$$

$$D = x' y_2' + y_1' y_2$$

PS $y_1 y_2$	J	K	D	J	K	D
00	0	1	1	0	1	0
01	0	0	1	1	1	1
10	0	1	1	0	1	0
11	0	0	0	1	1	0

Excitation table

for
CND
in 2
KND
- 10.5

② Output equations

$$Z = x y_1 y_2'$$

PS $y_1 y_2$	Z	
	$x=0$	$x=1$
00	0	0
01	0	0
10	0	1
11	0	0

can be
simplified
to 3
terms
using K-map

③ Next state equations

They are derived by substituting the excitation equations of each FF into its characteristic equation

JK FF: $Q(t+1) = K'Q + JQ'$

$$Y_2(t+1) = (x + y_2')y_1 + (xy_2)y_1' = x'y_1y_2 + xy_1'y_2$$

D FF: $Q(t+1) = D$

$$Y_2(t+1) = x'y_2' + y_1'y_2$$

④ State Table


Set symbols to states

$a=00$ $b=01$ $c=10$ $d=11$

PS	NS($Y_1 Y_2$) / output (z)	
$y_1 y_2$	$x=0$	$x=1$
00	01/0	00/0
01	01/0	11/0
10	01/0	00/1
11	10/0	00/0


PS	NS/output ($Y_1 Y_2 / z$)	
$y_1 y_2$	$x=0$	$x=1$
a	b/0	a/0
b	b/0	d/0
c	b/0	a/1
d	c/0	a/0

⑤ State diagram

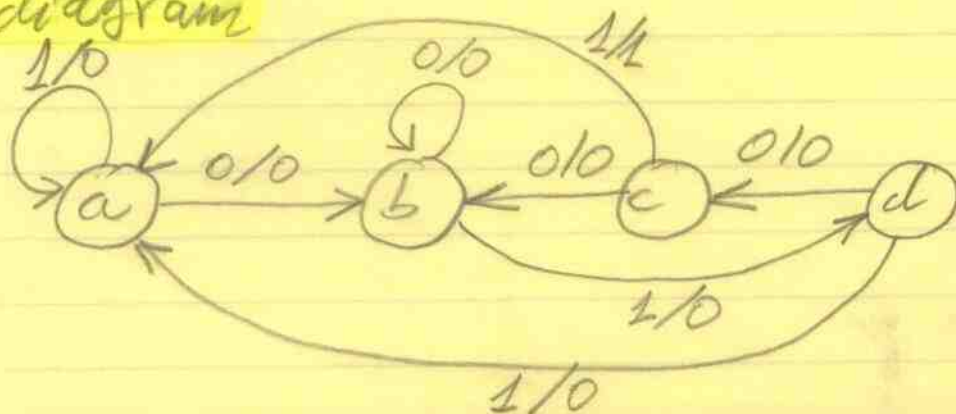

⑥ Timing diagram

-8-

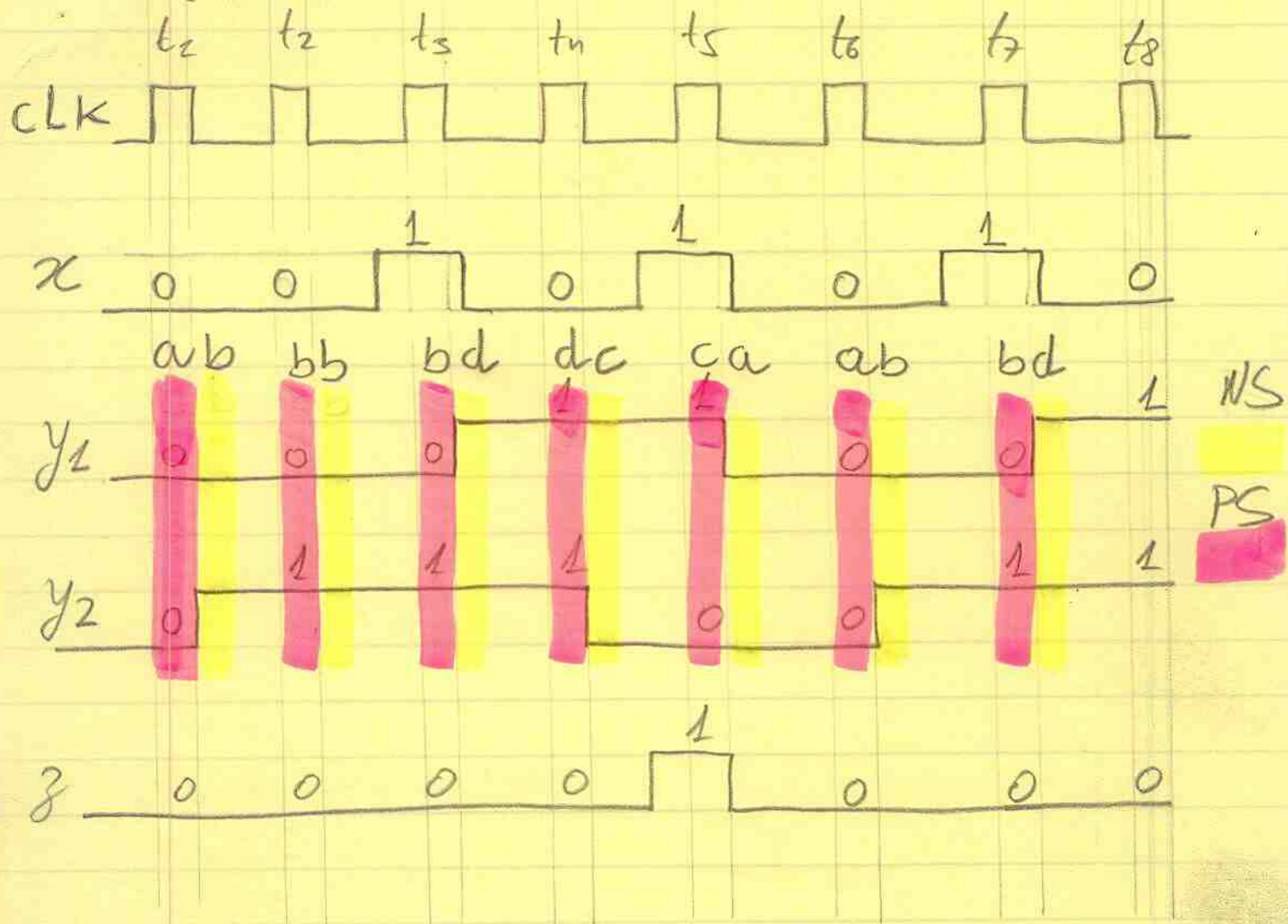

Comments:

- Timing diagram is ideal, no propagation delay
- Input counts for setup time and hold time
- Transitions on negative edge
- Input VS output

0	0	1	0	1	0	1	0
0	0	0	0	1	0	0	0

-9-

- This state machine discovers 0101 sequences.
- Present state is read before transition, while
- next state occurs after transition edge

Design example - Filter

Design spec.

Input is a sequence of 0's and 1's.

The output starts on the same value as input and changes its value only if a sequence of 3 consecutive pulses of opposite value occurs. Namely, the circuit filters sequences of length shorter than 3

input x:	0	0	1	0	1	0	1	1	1	0	0	0	1	1	1	0	1
output z:	0	0	0	0	0	0	0	0	1	1	1	0	0	0	1	1	1

x:	1	1	0	0	0	0	1	0	1	1	1	0	1	0	0	0	0
z:	1	1	1	1	0	0	0	0	0	0	1	1	1	1	1	0	0

Step ①: State diagram and table

① - Initial state, on 0 goto ②, on 1 goto ③

② - Reporting steady 0 sequence - output 0


③ - $\begin{matrix} -11 & +1 & 1 & -1 & - & -1 & 1 \end{matrix}$

④ - Indicate 1st 1 - output 0

⑤ - " " 0 - $\begin{matrix} -1 & 1 \end{matrix}$

⑥ - Indicate 2nd 1 - output 0 $\xrightarrow{\text{3rd 1}}$ ③

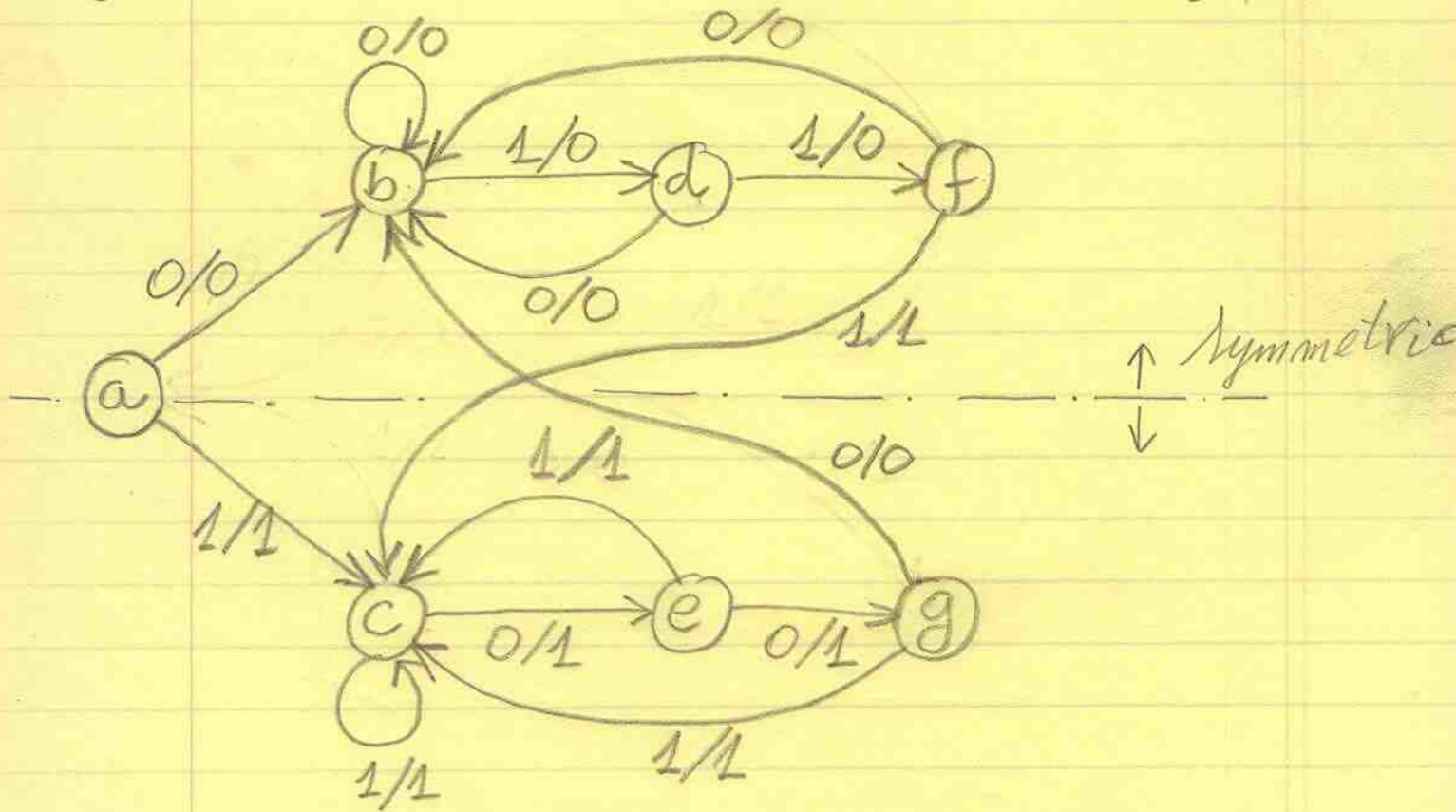⑦ - " " 0 - " 1 $\xrightarrow{\text{3rd 0}}$ ②



Symmetry! - good sanity check!

PS	NS/output (z)	
	$x=0$	$x=1$
a	b/0	c/1
b	b/0	d/0
c	e/1	c/1
d	b/0	f/0
e	g/1	c/1
f	b/0	c/1
g	b/0	c/1

Step (2) - State reduction $\{b\}$

a, f and g are equivalent $\{a, f, g\}, \{c\}, \{d\}, \{e\}$

PS	NS/output z	
	$x=0$	$x=1$
a	b/0	c/1
b	b/0	d/0
c	e/1	c/1
d	b/0	a/0
e	a/1	c/1

Step ③ - state assignment

Assignment requires 3 state variables and is arbitrary (synchronous) unlike asynchronous where race-free assignment is in order

PS $y_1 y_2 y_3$	NS($y_1 y_2 y_3$) / output (z)	
	$x=0$	$x=1$
000	001 / 0	010 / 1
001	001 / 0	011 / 0
010	100 / 1	010 / 1
011	001 / 0	000 / 0
100	000 / 1	010 / 1

Step ④ - Next state and output equations

$y_3 x$		00	01	11	10
$y_1 y_2$	00	0	1	0	0
	01	1	1	0	0
	11	X	X	X	X
	10	1	1	X	X

$$z = y_1 + y_3'x + y_2y_3'$$

$y_3 x$ $y_1 y_2$	00	01	11	10
00	1	0	1	1
01	0	0	0	1
11	x	x	x	x
10	0	0	x	x

$$Y_3(t+1) = y_1' y_2' x' + y_3 x' + y_2' y_3$$

$Y_1(t+1)$ and $Y_2(t+1)$ are derived similarly

$$\left. \begin{aligned} Y_1(t+1) &= y_2 y_3' x' \\ Y_2(t+1) &= y_2' x + y_3' x \end{aligned} \right\} \text{Homework}$$

Step ⑤ FlipFlop excitation equations

No general algorithm to decide on type of FF.

We use JK FF

$$Q(t+1) = K'Q + JQ'$$

$$Y_1(t+1) = y_2 y_3' x' = (y_2 y_3' x') y_1 + (y_2 y_3' x') y_1'$$

$$\Rightarrow K_1 = y_2' + y_3 + x, \quad J_1 = y_2 y_3' x'$$

-14-

$$Y_2(t+1) = y_2'x + y_3'x = y_2'x + y_2y_3'x + \cancel{y_2'y_3'x} = \text{absorption}$$

$$= (y_3'x)y_2 + (x)y_2'$$

$$\Rightarrow K_2 = (y_3'x)' = y_3 + x', \quad J_2 = x$$

$$Y_3(t+1) = y_1'y_2'x' + y_3x' + y_2'y_3 =$$

$$y_3(y_1'y_2'x' + x' + y_2') + y_3'(y_1'y_2'x') = \text{absorption}$$

$$= (x' + y_2')y_3 + (y_1'y_2'x')y_3'$$

$$\Rightarrow K_3 = (x' + y_2')' = x \cdot y_2, \quad J_3 = y_1'y_2'x'$$

Alternatively, excitation table conditions can be embedded directly into state transition table and then use K-map for each K_i and J_i

$Q(t) (y_i)$	$Q(t+1) (Y_i)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

DS $y_1 y_2 y_3$	WS ($y_1 y_2 y_3$)		$x=0$					
	$x=0$	$x=1$	J_1	K_1	J_2	K_2	J_3	K_3
000	001	010	0	X	0	X	1	X
001	001	011	0	X	0	X	X	0
010	100	010	1	X	X	1	0	X
011	001	000	0	X	X	1	X	0
100	000	010	X	1	0	X	0	X

$x=1$					
J_1	K_1	J_2	K_2	J_3	K_3
0	X	1	X	0	X
0	X	1	X	X	0
0	X	X	0	0	X
0	X	X	1	X	1
X	1	1	X	0	X

We can build K-maps $J_i(y_1, y_2, y_3, x)$ and $K_i(y_1, y_2, y_3, x)$ $i=1, 2, 3$ and derive excitation equation for each FF - Homework. This may yield simpler excitation equations

-16-

J_1 Map

$y_3 x$	00	01	11	10
$y_1 y_2$	00	0	0	0
01	1	0	0	0
11	X	X	X	X
10	X	X	X	X

K_1 map





$y_3 x$	00	01	11	10	
$y_1 y_2$	00	X	X	X	X
01	X	X	X	X	
11	X	X	X	X	
10	1	1	X	X	

$$J_1 = y_2 y_3' x'$$

$$K_1 = 1$$

(Simpler than $y_2' + y_3 + x$)

Step 6 - Circuit Logic diagram

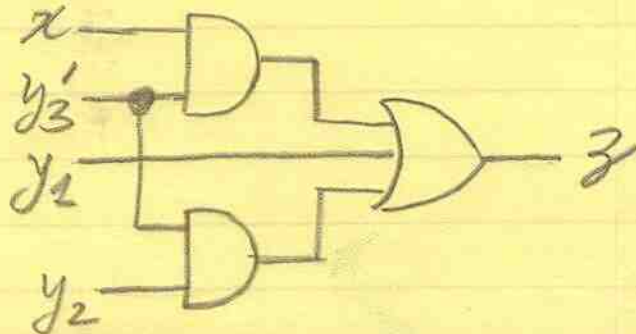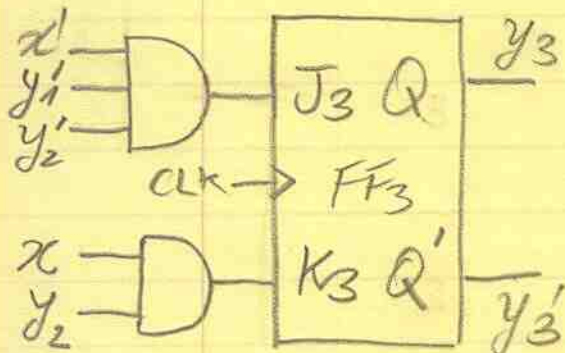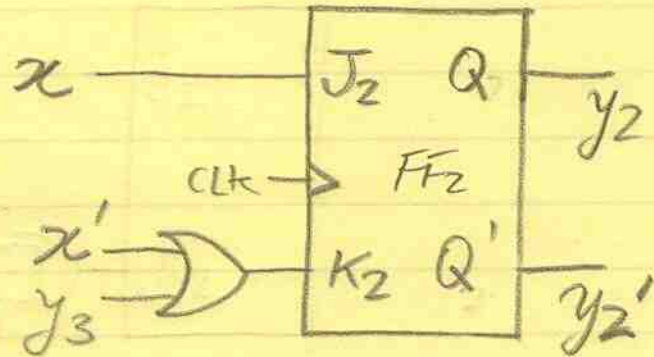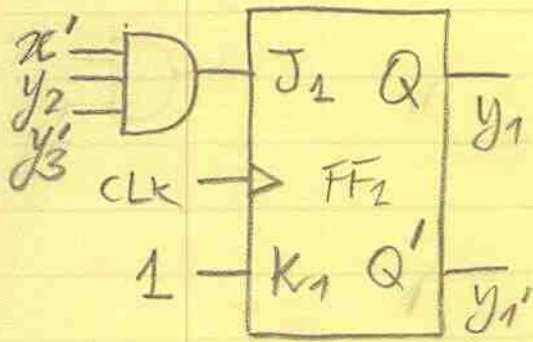

Important:

- 1- Circuit works properly if it preset to its initial state 000. This requires asynchronous inputs to FF (not studied)
- 2- If upon initialization in any of the invalid states (unused codes) the circuit goes to valid state (used code) within few pulses, this is called self-starting, which is okay but must be validated.
- 3- Otherwise, all unused states must be assigned with valid next state (e.g. a-000) on the expense of giving up the don't care (more complex excitation equations)

Homework: ^{self-starting} Verify from excitation equation